

11819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

22324

Instructions :

- (1) All Questions are compulsory.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.

- | | Marks |
|---|-------|
| 1. Attempt any FIVE of the following : | 10 |
| (a) Define active power and reactive power for RLC series circuit. | |
| (b) Draw impedance triangle and voltage triangle for RL series circuit. | |
| (c) Define susceptance and admittance for parallel circuit. | |
| (d) Define quality factor for parallel resonance and write its mathematical expression. | |
| (e) Draw sinusoidal waveform of 3 phase emf and indicate the phase sequence. | |
| (f) Write the procedure of converting a current source into voltage source. | |
| (g) State superposition theorem applied to d.c. circuits. | |
| 2. Attempt any THREE of the following : | 12 |
| (a) Draw a circuit diagram of R.C. series circuit. Draw impedance triangle and power triangle for same circuit. | |
| (b) Two circuits the impedance of which are given by $Z_1 = 6 + j8$ ohm and $Z_2 = 8 - j6$ ohm are connected in parallel. If the applied voltage to the combination is 100 V. Find (i) Current and power factor at each branch (ii) Overall current and power factor of the combination. (iii) Power consumed by each impedance. Draw phasor diagram. | |

- (c) State any four advantages of polyphase circuits over single phase circuit.
- (d) Using mesh analysis, find loop currents I_1 and I_2 in the circuit, as shown in

fig no. 1

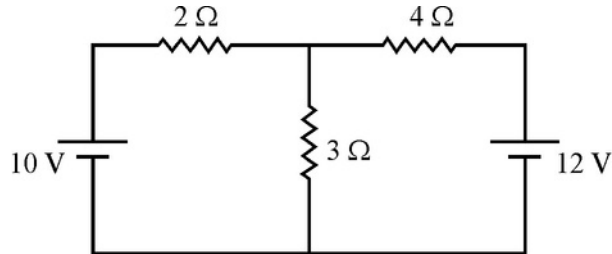


Fig. 1

3. Attempt any THREE of the following :

12

- (a) Derive the expression for resonance frequency for a RLC series circuits.
- (b) Compare series resonance to parallel resonance on the basis of
- | | |
|------------------------|--------------------|
| (i) Resonant Frequency | (ii) Impedance |
| (iii) Current | (iv) Magnification |
- (c) Compare star & delta connection. (any four points)
- (d) By using Nodal analysis calculate the current in $110\ \Omega$ resistor and p.d. across $110\ \Omega$ resistor as shown in fig. no. 2.

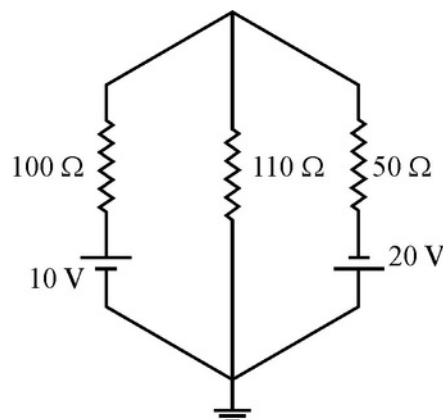


Fig. 2

- (e) Convert following circuit as shown in fig. no. 3 into Thevenins circuit across A & B.

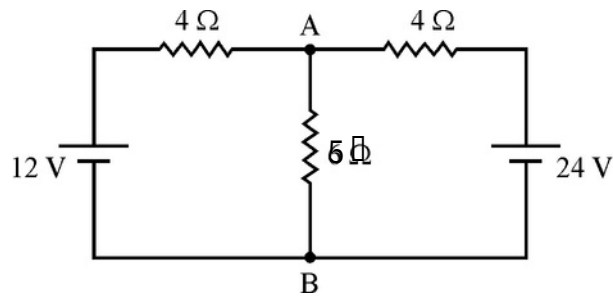


Fig. 3

4. Attempt any THREE of the following : 12

(a) A resistance of 100Ω , an inductance of 0.2H and capacitance of $150 \mu\text{F}$ are connected in series across 230 V , 50 Hz ac supply. Calculate the current drawn by the circuit, power factor of the circuit, its nature and power consumed by the circuit. Define :

(b)

(i) Admittance

(ii) Susceptance

(iii) Conductance (iv) State the units for admittance & conductance
Delta connected induction motor is supplied by 3 phase, 400 V , 50 Hz . Supply the line

(c) current is 43.03 amp and the total power from the supply is 24 kW . Find resistance and reactance per phase of motor. Derive the formulae for star to delta transformation.

(d)

5. Attempt any TWO of the following : 12

(a) A choke coil has a resistance of 4Ω and inductance of 0.07 H is connected in parallel with another coil of resistance 10Ω and inductance of 0.12 H . The combination is connected to 230 V , 50 Hz supply. Determine total current and current through each branch.

- (b) Determine the current in $40\ \Omega$ and $10\ \Omega$ as shown in fig. no. 4 by node voltage analysis method.

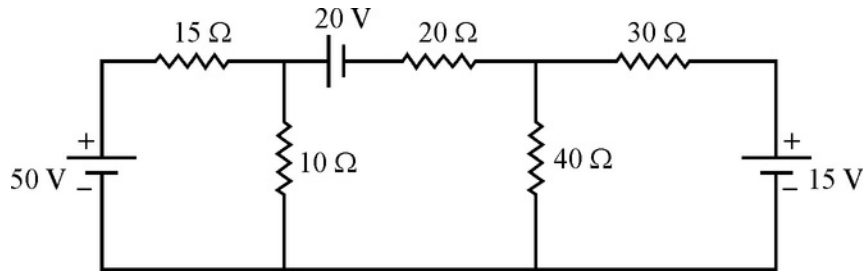


Fig. 4

- (c) Use Norton's theorem to find the current through $3\ \Omega$ resistance, for the circuit shown in fig. no. 5

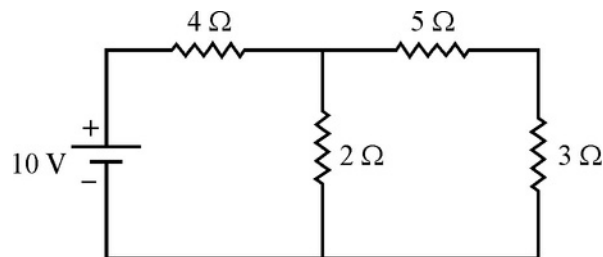


Fig. 5

6. Attempt any TWO of the following :

12

- (a) Voltage across a coil is $146.2\ \text{V}$ and across a series resistance is $150\ \text{V}$, when they are connected across $220\ \text{V}$, $50\ \text{Hz}$ supply. If supply current is $10\ \text{amp}$, find
- Resistance of coil
 - Inductance of coil
 - Power consumed by coil
 - Power factor of total circuit
- (b) In a 3 phase star connected system, derive the relationship $V_L = \sqrt{3} V_{ph}$.
- (c) State the Thevenin's theorem. Also write stepwise procedure for applying Thevenin's theorem to simple circuits.

Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

1 Attempt any FIVE of the following: 10

1 a) Define active power and reactive power for RLC series circuit.

Ans:

Active Power (P):

Active power (P) is given by the product of voltage, current and the cosine of the phase angle between voltage and current. 1 mark

Unit: watt (W) or kilo-watt (kW) or Mega-watt (MW).

$$P = VI \cos\phi = I^2R \text{ watt}$$

Reactive Power (Q):



Reactive power (Q) is given by the product of voltage, current and the sine of the phase angle between voltage and current. 1 mark

Unit: volt-ampere-reactive (VAR), or kilo-volt-ampere-reactive (kVAR) or Mega-volt-ampere-reactive (MVAR)

$$Q = VI \sin\phi = IX \text{ volt-amp-reactive.}$$

1 b) Draw impedance triangle and voltage triangle for RL series circuit.

Ans:

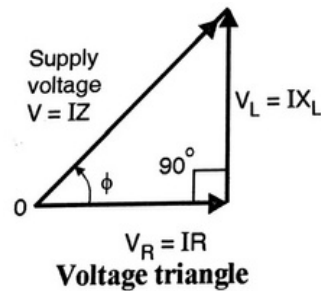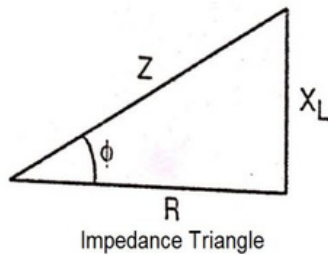

1 mark for
each triangle
= 2 marks

1 c) Define susceptance and admittance for parallel circuit.

Ans:

Admittance (Y):

Admittance is defined as the ability of the circuit to carry (admit) alternating current through it. It is the reciprocal of impedance Z. i.e $Y = 1/Z$. 1 mark

For parallel circuit consisting two branches having impedances Z_1 and Z_2 in parallel, the equivalent impedance of parallel combination is given by, (Equations are optional)

— — —

where, Y is the equivalent admittance of the parallel circuit

Y_1 and Y_2 are the admittances of the two branches respectively.

If the equivalent impedance is expressed as _____, then the admittance is obtained as,

— — — — —
— — — — —

Susceptance (B):

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

Susceptance is defined as the imaginary part of the admittance.

It is expressed as,

1 mark

$$B = \frac{1}{X_c}$$

In DC circuit, the reactance is absent, hence $X = 0$ and susceptance equals to zero.

- 1 d) Define quality factor for parallel resonance and write its mathematical expression.

Ans:

Quality Factor of Parallel AC Circuit at resonance:

The quality factor or Q-factor of parallel circuit is defined as the ratio of the current circulating between two branches of the circuit to the current taken by the parallel circuit from the source.

It is the current magnification in parallel circuit.

Formula:

$$\text{Quality factor (Q-factor)} = \text{Current magnification} = \frac{I_{\text{branch}}}{I_{\text{total}}}$$

1 mark


Where, R is the resistance of an inductor in Ω ,

L is the inductance of an inductor in henry,

C is capacitance of capacitor in farad,

- 1 e) Draw sinusoidal waveform of 3 phase emf and indicate the phase sequence.

Ans –

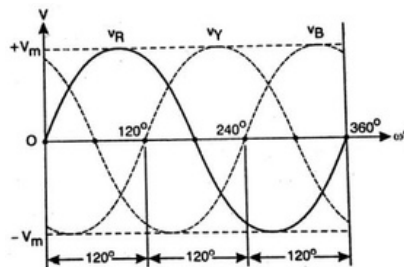

1½ marks for waveform

½ mark for phase sequence

Phase sequence is R-Y-B.

- 1 f) Write the procedure of converting a given current source into voltage source.

Ans:


Conversion of current source into equivalent voltage source:

Let I_S be the practical current source magnitude and

Z_I be the internal parallel impedance.

V_S be the equivalent practical voltage source magnitude and

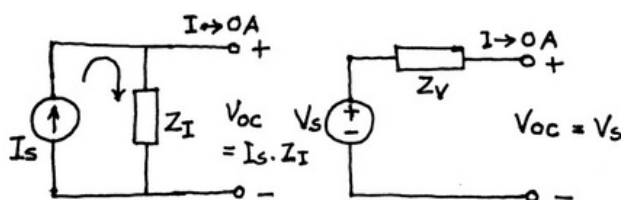Z_V be the internal series impedance of the voltage source.



1 mark for diagram


1 mark for description

The open circuit terminal voltage of current source is $V_{oc} = I_S \times Z_I$

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

The open circuit terminal voltage of voltage source is $V_{OC} = V_S$
Therefore, we get $V_S = I_S \square Z_I$ (1)

OR

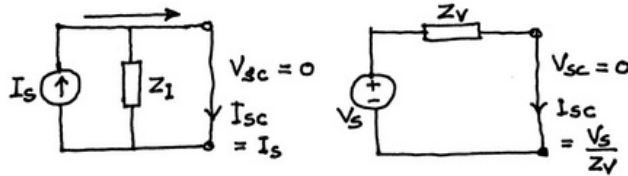

The short circuit output current of current source is $I_{SC} = I_S$
The short circuit output current of voltage source is $I_{SC} = V_S / Z_V$
Therefore, we get $I_S = V_S / Z_V$ (2)

On comparing eq. (1) and (2), it is clear that $Z_I = Z_V = Z$ (3)

Thus the internal impedance of both the sources is same, and the magnitudes of the source voltage and current are related by Ohm's law, $V_S = I_S \square Z_I$

- 1 g) State superposition theorem applied to the d.c. circuits.

Ans:

Superposition Theorem applied to D.C. circuits:

Superposition theorem states that in any linear, bilateral, multisource network, the response (voltage across any element or current through any element) of any branch is equal to the algebraic sum of the responses produced in it with each source acting alone, while the other sources are replaced by their internal resistances.

OR




Any other equivalent valid statement

- 2 Attempt any **THREE** of the following:

12

- 2 a) Draw a circuit diagram of R.C. series circuit. Draw impedance triangle and power triangle for same circuit.

Ans –

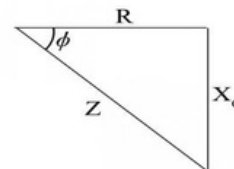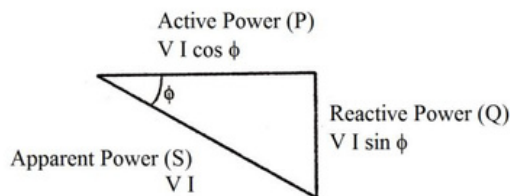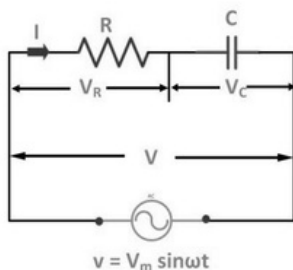


1 mark for
circuit
½ mark for
each of
power &
voltage
triangle

- 2 b) Two circuits the impedance of which are given by $Z_1 = 6 + j8$ ohm and $Z_2 = 8 - j6$ ohm are connected in parallel. If the applied voltage to the combination is 100V, Find:
(i) Current and power factor at each branch.
(ii) Overall current and power factor of the combination.
(iii) Power consumed by each impedance. Draw phasor diagram.

Ans:

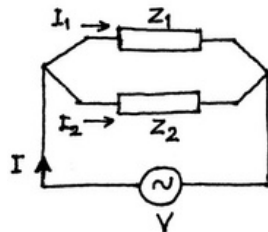**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**



Data given:

□
□

1 mark

(i) Current and power factor at each branch:

Current of branch 1: $I_1 = V/Z_1 = \text{————}$

Power factor of branch 1: $\cos(53.13^\circ) = \mathbf{0.6 \text{ lagging}}$

Current of branch 2: $I_2 = V/Z_2 = \text{————}$

Power factor of branch 2: $\cos(36.87^\circ) = \mathbf{0.8 \text{ leading}}$

1 mark

(ii) Overall current and power factor of the combination:

Over all current $I = I_1 + I_2 =$

Overall power factor: $\cos(8.13^\circ) = \mathbf{0.98 \text{ lagging}}$

1 mark

(iii) Power consumed by each impedance:


Power consumed by $Z_1 : V \cdot I_1 \cdot \cos\phi_1 = (100)(10)\cos(53.13^\circ) = \mathbf{600W}$

$$I_1^2 R_1 = (10)^2(6) = 600W$$

Power consumed by $Z_2 : V \cdot I_2 \cdot \cos\phi_2 = (100)(10)\cos(36.87^\circ) = \mathbf{800W}$

$$I_2^2 R_2 = (10)^2(8) = 800W$$

(iv) Phasor diagram:

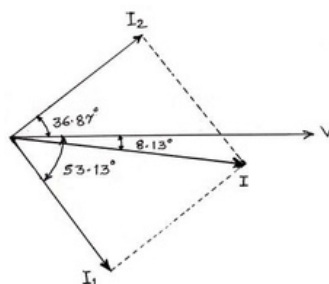

1 mark

2 c) State any four advantages of polyphase circuits over single phase circuit.

Ans:

Advantages of polyphase (3-phase) circuits over Single-phase circuits:

- i) Three-phase transmission is more economical than single-phase transmission. It requires less copper material. 1 mark for
- ii) Parallel operation of 3-phase alternators is easier than that of single-phase alternators. each of any four
- iii) Single-phase loads can be connected along with 3-ph loads in a 3-ph system. = 4 marks

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

- iv) Instead of pulsating power of single-phase supply, constant power is obtained in 3-phase system.
- v) Three-phase induction motors are self-starting. They have high efficiency, better power factor and uniform torque.
- vi) The power rating of 3-phase machine is higher than that of 1-phase machine of the same size.
- vii) The size of 3-phase machine is smaller than that of 1-phase machine of the same power rating.
- viii) For same power rating, three-phase motors are cheaper than the single-phase motors.

2 d) Using mesh analysis, find loop currents I1 and I2 in the circuit, as shown in fig. no. 1


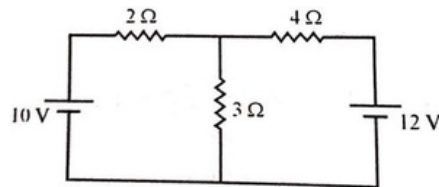


Fig. 1

Ans:

Mesh Analysis:

i) There are two meshes in the network.

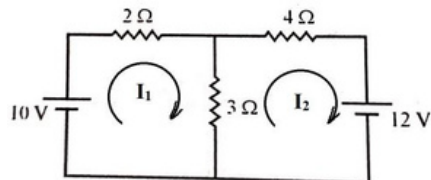

ii) Mesh currents I1 and I2 are marked clockwise as shown.

iii) By tracing mesh 1 clockwise, KVL equation is,

By tracing mesh 2 clockwise, KVL equation is, 1 mark

iv) Expressing eq.(1) and (2) in matrix form, 1 mark

$$* \quad + [\quad] * \quad +$$

By Cramer's rule,

$$\frac{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}} = \frac{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}$$

1 mark

$$\frac{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}} = \frac{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}$$

1 mark

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

3 Attempt any THREE of the following: 12

3 a) Derive the expression for resonance frequency for a RLC series circuit.

Ans:

Resonant Frequency of Series RLC Circuit:

In RLC series circuit the resonance occurs when the inductive reactance (XL) becomes equal to the capacitive reactance (XC).

Inductive reactance is given by $X_L = 2\pi fL$

Capacitive reactance is given by $X_C = \frac{1}{2\pi fC}$

The inductive reactance (XL) becomes equal to capacitive reactance (XC) only at one particular frequency, which is known as resonant frequency and it is denoted by fr.

Hence at resonance,

$$X_L - X_C = 0$$

$$X_L = X_C$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

1 mark for equations of reactances

1 mark for resonance condition

1 mark

Rearranging above equation,
We get,

$$(f_r)^2 = \frac{1}{4\pi^2 LC}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \text{ Hz} \quad \text{OR} \quad \omega_r = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

1 mark

3 b) Compare series resonance to parallel resonance on the basis of
(i) Resonant frequency (ii) Impedance (iii) Current (iv) Magnification

Ans:

Parameter	Series Resonant Circuit	Parallel Resonant Circuit
Resonant frequency	$\frac{1}{2\pi\sqrt{LC}}$	$\frac{1}{2\pi\sqrt{LC}}$
Impedance	Minimum $Z = R$ ohms	Maximum $Z = \frac{R}{1 - \omega^2 LC}$
Current	Maximum $I = \frac{V}{R}$	Minimum $I = \frac{V}{Z}$
Magnification	Voltage magnification	Current magnification

1 mark for each point = 4 marks

3 c) Compare star and delta connection. (Any four points)

Ans:

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

Parameter	Star Connection	Delta Connection
Basic definition	One terminal of each of the three branches are connected together to form a common point. Such a connection is known as Star Connection	The three branches of the network are connected in such a way that it forms a closed loop. Such a connection is known as Delta Connection
Connection terminals	The similar ends of the three coils are connected together to form a common point.	The end of each coil is connected to the starting point of the other coil that opposite terminals of the coils are connected together to form a closed loop.
Neutral point	Neutral or the star point exists in the star connection.	Neutral point does not exist in the delta connection.
Relation between line and phase current	Line current is equal to the Phase current.	Line current is equal to $\sqrt{3}$ times the Phase Current.
Relation between line and phase voltage	Line voltage is equal to $\sqrt{3}$ times the Phase Voltage	Line voltage is equal to the Phase voltage.
Diagram		

1 mark for each of any four points = 4 marks

- 3 d) By using nodal analysis, calculate the current in 110Ω resistor and p.d. across 110Ω resistor as shown in fig. no. 2

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**


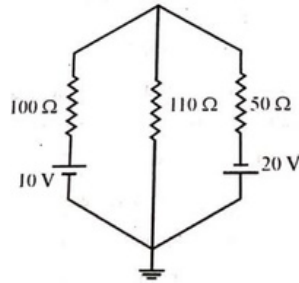


Fig. 2

Ans:

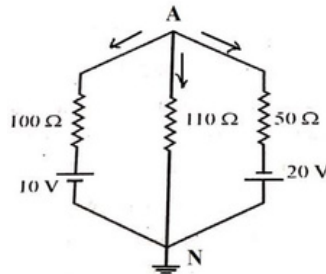

1 mark for
diagram with
currents

By applying KCL at node A, the node voltage equation can be written as:

$$\frac{V_A - 10}{100} + \frac{V_A - 0}{110} + \frac{V_A - 20}{50} = 0$$

1 mark

P. D. across 110Ω resistor is

(Terminal N is at higher potential than terminal A)

1 mark

Current flowing through 110Ω is given by,

$$I = \frac{V_A - 0}{110}$$

1 mark

I = 0.0697A flowing from terminal N to A

3 e) Convert following circuit as shown in fig. no. 3 into Thevenin's circuit across A & B.


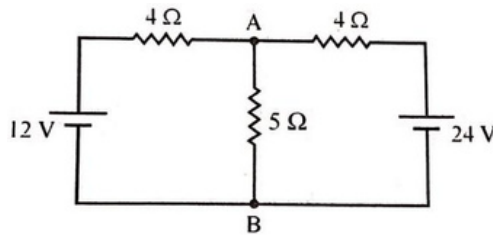


Fig. 3

Ans:

Determination of Thevenin's Equivalent Voltage Source (V_{Th}):

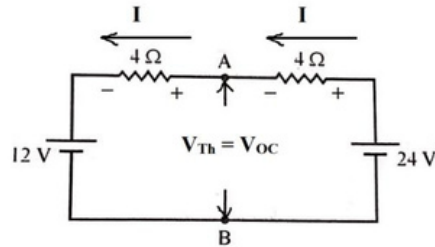**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**



½ mark for figure

Thevenin's equivalent voltage source V_{Th} is the open circuit voltage across the load terminals A-B due to internal sources, as shown in the figure.

By tracing loop in anti-clockwise direction, the voltage equation can be written as:

$$24 - 4I - 4I - 12 = 0$$


$$\text{Circuit current } I = (24-12)/8 = 1.5 \text{ A}$$

The Thevenin's equivalent voltage is given by,

$$\begin{aligned} V_{Th} = V_{OC} &= 24 - 4I = 24 - 6 = \mathbf{18 \text{ volt}} \\ &= 12 + 4I = 12 + 6 = \mathbf{18 \text{ volt}} \end{aligned}$$

1 mark

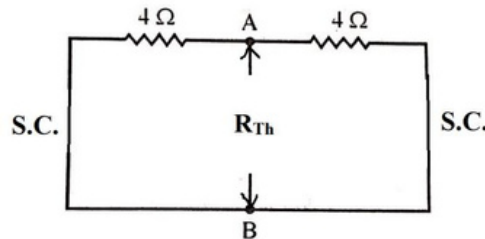Determination of Thevenin's Equivalent Resistance (R_{Th}):



½ mark for figure


Thevenin's equivalent resistance is the resistance seen between the open-circuited load terminals while looking back into the network, with internal independent voltage sources replaced by short-circuit and independent current sources replaced by open-circuit, as shown in the following figure.



1 mark

Thevenin's Equivalent Circuit:

Thevenin Equivalent Circuit

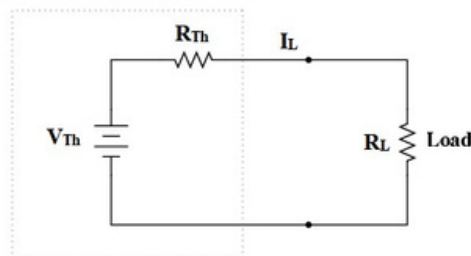

1 mark

$$V_{Th} = 18V, \quad R_{Th} = 2 \Omega, \quad R_L = 5 \Omega$$

4 Attempt any **THREE** of the following.

12

4 a) A resistance of 100Ω , an inductance of 0.2 H and capacitance of $150 \mu\text{F}$ are connected in series across 230V , 50 Hz ac supply. Calculate the current drawn by the circuit, power factor of the circuit, its nature and power consumed by the circuit.

Ans:

Given: $R = 100 \Omega$, $L = 0.2\text{H}$, $C = 150 \mu\text{F} = 150 \times 10^{-6}\text{F}$, $V = 230\text{V}$, $f = 50 \text{ Hz}$

Model Answers

Winter – 2018 Examinations

Subject & Code: Electrical Circuits (22324)

$$X_L = 2 \pi f L = 2 \times \pi \times 50 \times 0.2 = 62.83 \Omega$$

$$X_C = 1/(2 \pi f C) = 1/(2 \times \pi \times 50 \times 150 \times 10^{-6}) = 21.22 \Omega$$

$$\text{Impedance } = Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{100^2 + (62.83 - 21.22)^2} = \mathbf{108.31 \Omega \text{ OR}}$$
$$= 100 + j(62.83 - 21.22) = (100 + j41.61) = \mathbf{108.31 \angle 22.59^\circ \Omega}$$

1 mark

$$(1) \text{ Total current } = I = V/Z = 230 \angle 0^\circ / 108.31 \angle 22.59^\circ = \mathbf{2.123 - 22.59^\circ \text{ A}}$$

1 mark

$$(2) \text{ Power factor } = \cos \phi = R/Z = 100/108.31 = \mathbf{0.923 \text{ lagging OR}}$$

$$= \cos(22.59^\circ) = \mathbf{0.923 \text{ lagging}}$$

1 mark

(3) Nature of power factor is **lagging**.

$$(4) P = I^2 R = 2.123^2 \times 100 = \mathbf{450.7 \text{ watt}} \quad \mathbf{OR}$$

1 mark

$$P = V I \cos \phi = 230 \times 2.123 \times 0.923 = \mathbf{450.7 \text{ watt}}$$

- 4 b) Define: (i) Admittance (ii) Susceptance
(iii) Conductance (iv) State the units of admittance and conductance

Ans:

(i) Admittance (Y):

Admittance is defined as the ability of the AC circuit to carry (admit) alternating current. It is also defined as reciprocal of impedance (Z).

$$\text{Admittance (Y)} = \frac{1}{Z} \text{ mho } (\Omega^{-1})$$

(ii) Susceptance (B):

It is imaginary part of the admittance (Y). It is defined as the ability of the purely reactive circuit (purely capacitive or purely inductive) to admit alternating current.

1 mark

OR

It is ratio of reactance (X) to squared impedance (Z).

In general, Susceptance (B) — siemen

(iii) Conductance (G):

It is defined as the real part of the admittance (Y). It is also defined as the ability of the purely resistive circuit to pass the alternating current.

OR

It is the ratio of resistance (R) to squared impedance (Z)

$$\text{Conductance (G)} = \frac{1}{Z^2} R \text{ siemen}$$

(iv) Units of admittance and conductance:

Unit of Admittance (Y) = **mho**

1 mark

Unit of Conductance (G) = **siemen**

- 4 c) Delta connected induction motor is supplied by 3 phase 400V, 50 Hz supply the line current is 43.03 amp and the total power from the supply is 24 kW. Find the resistance and reactance per phase of the motor.

Ans:

Data Given:

$$V_L = 400V, \quad 3 \phi \text{ (Delta connected)} \quad I_L = 43.03 \text{ A}$$

$$P = 24 \text{ kW} \quad f = 50 \text{ Hz}$$

$$\text{In Delta connection} \quad I_L = \sqrt{3} I_{Ph}$$

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

$$I_{ph} = \frac{P}{\sqrt{3} V_L}$$

$$I_{ph} = \frac{P}{\sqrt{3} V_L}$$

$$I_{ph} = 24.84 \text{ A}$$

½ mark

In Delta connection $V_L = V_{ph}$
Hence,

$$V_{ph} = V_L = 400 \text{ V}$$

Total three-phase power supplied to motor is given by,

$$P = 3 V_{ph} I_{ph} \cos \phi$$

$$\cos \phi = \frac{P}{3 V_{ph} I_{ph}} = \frac{P}{3 \times 400 \times 24.84} = 0.805 \text{ lagging}$$

½ mark

i) Impedance per phase Z_{ph} :

$$Z_{ph} = \frac{V_{ph}}{I_{ph}}$$

$$Z_{ph} = \frac{400}{24.84} = 16.10 \Omega$$

Impedance per phase **$Z_{ph} = 16.10 \Omega$**

1 mark

ii) Resistance per Phase R_{ph} :

$$\cos \phi = \frac{R_{ph}}{Z_{ph}} \quad R_{ph} = Z_{ph} \cos \phi$$

$$R_{ph} = 16.10 \times 0.805$$

$$R_{ph} = 12.96 \Omega$$

1 mark

iii) Reactance per Phase X_{Lph} :

$$X_{Lph} = \sqrt{Z_{ph}^2 - R_{ph}^2}$$

$$X_{Lph} = \sqrt{16.10^2 - 12.96^2} = 9.55 \Omega$$

$$X_{Lph} = 9.55 \Omega$$


1 mark

(Correct solution by any other method may please be considered)

4 d) Derive the formulae for star to delta transformation.

Ans:

Star-delta Transformation:

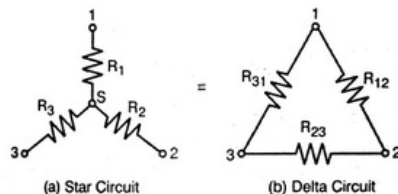

If the star circuit and delta circuit are equivalent, then the resistance between any two terminals of the circuit must be same.

For star circuit, resistance between terminals 1 & 2, say R_{1-2}

For delta circuit, resistance between terminals 1 & 2, R_{1-2}

Similarly, the resistance between terminals 2 & 3 can be equated as,

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

And the resistance between terminals 3 & 1 can be equated as,

Subtracting eq. (2) from eq.(1),

Adding eq.(3) and eq.(4) and dividing both sides by 2,

$$[\text{_____}]$$

Similarly, we can obtain,

$$[\text{_____}]$$

$$[\text{_____}]$$

Multiplying each two of eq.(5), (6) and (7),

$$[\text{_____}]$$

$$[\text{_____}]$$

$$[\text{_____}]$$

Adding the three equations (8), (9) and (10),

$$\text{_____}$$

$$\text{_____}$$

$$\text{_____}$$

Dividing eq.(11) by eq.(6), (dividing by respective sides)

$$\text{_____}$$

Similarly, we can obtain,

$$\text{_____}$$

$$\text{_____}$$

Thus using known star connected resistors R1, R2 and R3, the unknown resistors R12, R23 and R31 of equivalent delta connection can be determined.

1 mark for
(eq.5, 6 & 7)

1 mark for
(eq.8, 9 &
10)

1 mark for
eq. 11

1 mark for
(eq. 12, 13 &
14)

Model Answers

Winter – 2018 Examinations

Subject & Code: Electrical Circuits (22324)

5 Attempt any TWO of the following: 12

5 a) A choke coil has a resistance of $4\ \Omega$ and inductance of 0.07H is connected in parallel with another coil of resistance $10\ \Omega$ and inductance 0.12H . The combination is connected to 230V , 50Hz supply. Determine total current and current through each branch.

Ans:

Data Given: $R_1 = 4\ \Omega$ $L_1 = 0.07\text{H}$ $R_2 = 10\ \Omega$ $L_2 = 0.12\text{H}$ $V = 230\text{V}$, $f = 50\text{Hz}$ ½ mark for each of XL1 & XL2
 $X_{L1} = 2\pi fL_1 = 2(50)(0.07) = 21.99\ \Omega$
 $X_{L2} = 2\pi fL_2 = 2(50)(0.12) = 37.7\ \Omega$ 1 mark
 $Z_1 = R_1 + jX_{L1} = (4 + j21.99) = 22.35\ \angle 79.7^\circ\ \Omega$ 1 mark
 $Z_2 = R_2 + jX_{L2} = (10 + j37.7) = 39.75\ \angle 75.144^\circ\ \Omega$

Branch 1 current is given by, 1 mark

$$I_1 = \frac{230}{22.35} = 10.3 - j79.7\ \text{A} = (1.84 - j10.13)\ \text{A}$$

Branch 2 current is given by,

$$I_2 = \frac{230}{39.75} = 5.89 - j75.144\ \text{A} = (1.51 - j5.7)\ \text{A} \quad \text{1 mark}$$

Total current is,

$$I = I_1 + I_2 = (1.84 - j10.13) + (1.51 - j5.7)$$

$$I = (3.35 - j15.825)\ \text{A} = 16.17\ \angle -78.04^\circ\ \text{A} \quad \text{1 mark}$$

5 b) Determine the current in $40\ \Omega$ and $10\ \Omega$ as shown in fig. no. 4 by node voltage analysis method.


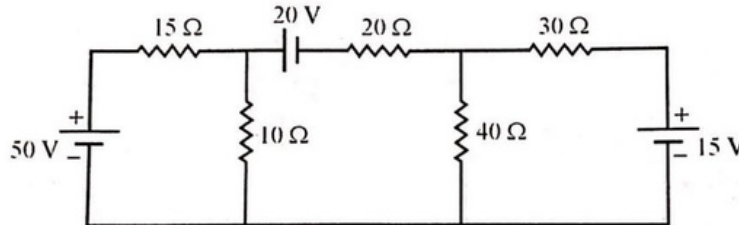


Fig. 4

Ans:

Node Voltage Analysis Method:

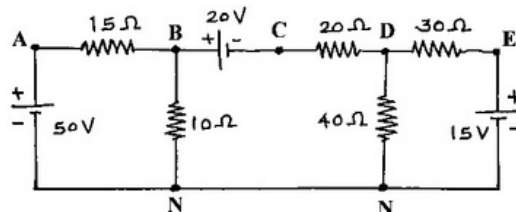Step I: Mark the nodes and reference node.




1 mark for node identification

Let the nodes be A, B, C, D, E and reference node is N.
From the above circuit diagram we can write,

Only two unknown voltages are V_B and V_D .

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

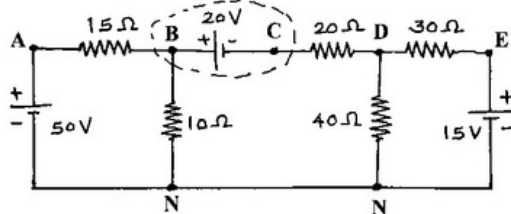Step II: Apply KCL at nodes with unknown voltages



Since there is a voltage source of 20V between nodes B and C, for writing KCL equations, let us treat nodes B and C with source as “Supernode”, encircled by dotted line.

By KCL at this supernode, we can write

$$\underline{\hspace{2cm}} \quad \underline{\hspace{2cm}} \quad \underline{\hspace{2cm}}$$

$$[\text{---} \text{---} \text{---}] \text{---} \text{---} \quad [\text{---}]$$

1 mark for eq. (i)

By KCL at node D, we write

$$\underline{\hspace{2cm}} \quad \underline{\hspace{2cm}} \quad \underline{\hspace{2cm}}$$

$$[\text{---}] \text{---} \text{---} \quad [\text{---} \text{---} \text{---}]$$

1 mark for eq. (ii)

Step III: Solving Simultaneous equations

Expressing eq. (i) and (ii) in matrix form,

$$* \quad \quad \quad + [\quad] * \quad \quad +$$

By Cramer's rule,

$$\frac{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}} = \underline{\hspace{2cm}}$$

$$\frac{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}} = \underline{\hspace{2cm}}$$

1 mark for stepwise solution for V_B and V_D

Step IV: Solving for currents

Current in 40Ω resistor is given by,

$$\underline{\hspace{2cm}}$$

1 mark

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

Current in 10Ω resistor is given by,

1 mark

- 5 c) Use Norton's theorem to find the current through 3Ω resistance, for the circuit shown in fig. no. 5


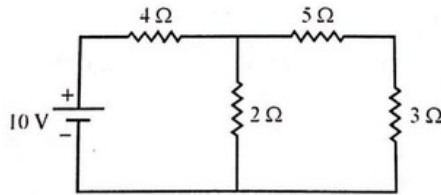


Fig. 5

Ans:

Solution by Norton's Theorem:

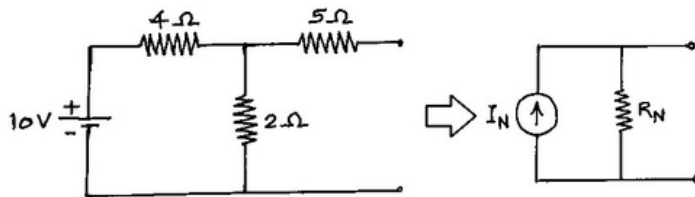According to Norton's theorem, the circuit between load terminals excluding load resistance can be represented by simple circuit consisting of a current source I_N in parallel with a resistance R_N , as shown in the following figure.




1 mark

Determination of Norton's Equivalent Current Source

(I_N): Norton's equivalent current source I_N is the current flowing through a short-circuit across the load terminals due to internal sources, as shown in fig.(a).

Total resistance across 10V source is,

_____ Ω

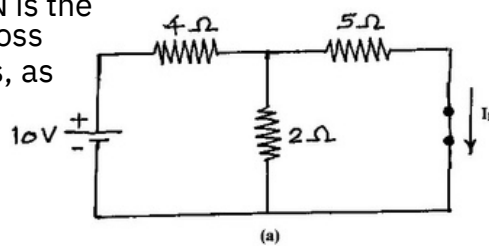

marks for
stepwise
solution of I_N
with circuit
diagram


Therefore, current supplied by source,

The resistances 2Ω and 5Ω are in parallel. By current division, the current flowing through 5Ω is same as I_N .

Determination of Norton's Equivalent

Resistance (R_N):

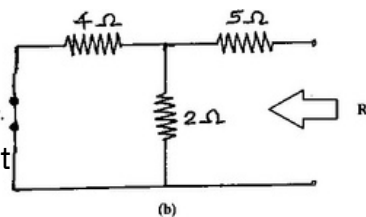Norton's equivalent resistance is the resistance seen between the load terminals while looking back into the network, with internal independent voltage sources replaced by short-circuit and independent current sources replaced by open-circuit. Referring to fig.(b),




1 mark for
stepwise
solution of
 R_N

1 mark for
equivalen

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

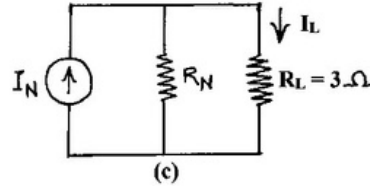Determination of Load Current (IL):
Referring to fig.(c), the load current is



circuit
1 mark for IL

6 Attempt any TWO of the following:


12

- 6 a) Voltage across a coil is 146.2V and across series resistance is 150V, when they are connected across 220V, 50Hz supply. If supply current is 10 amp, find:
- Resistance of coil
 - Inductance of coil
 - Power consumed by coil
 - Power factor of total circuit

Ans:

Data given:

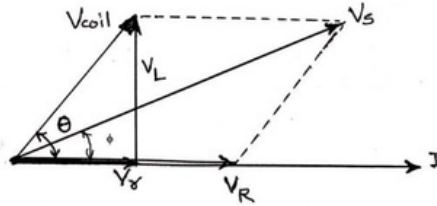$V_S = 220V, f = 50Hz, V_{Coil} = 146.2V, V_R = 150V, I = 10A$



1 mark for phasor diagram

Referring to the phasor diagram above,

$\sqrt{\quad}$

1/2 mark for \square

- \square Voltage across resistance of coil, $V_r = V_{Coil} \cos \square = (146.2)(0.1032) = 15.087$ volt 1/2 mark
- \square Voltage across inductance of coil, $V_L = V_{Coil} \sin \square = (146.2)\sin(\quad) = 145.42$ volt 1/2 mark
- (i) **Resistance of Coil:**
- (ii) Resistance of coil, $r = V_r / I = 15.087/10 = \mathbf{1.5087\Omega}$ 1/2 mark for r
- Inductance of Coil:**
Inductive Reactance of Coil, $X_L = V_L / I = 145.42/10 = 14.54\Omega$
 \square Inductance of Coil, $L = X_L / (2\pi f) = 14.54 / (2 \times 50) = \mathbf{0.0462H}$ 1 mark for L
- (iii) **Power consumed by coil:**
- (iv) $P = I^2 r = (10)^2(1.5087) = \mathbf{150.87}$ watt 1 mark for P
- Power factor of total circuit:**
Referring to the phasor diagram above,
 $V_S \cos \square = (V_r + V_R)$
 \square Power factor of total circuit, $\cos \square = (V_r + V_R) / V_S = (15.087 + 150) / 220$ 1 mark for total pf
 $\square \cos \square = \mathbf{0.75}$ lagging

- 6 b) In a 3 phase star connected system, derive the relationship $\bar{V}_L = \sqrt{3} V_{ph}$.

**Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)**

Ans:

Relationship Between Line voltage and Phase Voltage in Star Connected System:

Let V_R, V_Y and V_B be the phase voltages.
 V_{RY}, V_{YB} and V_{BR} be the line voltages.

The line voltages are expressed as:

$$V_{RY} = V_R - V_Y$$

$$V_{YB} = V_Y - V_B$$


$$V_{BR} = V_B - V_R$$

In phasor diagram, the phase voltages are drawn first with equal amplitude and displaced from each other by 120° . Then line voltages are drawn as per the above equations. It is seen that the line voltage V_{RY} is the phasor sum of phase voltages V_R and $-V_Y$. We know that in parallelogram, the diagonals bisect each other with an angle of 90° .

Therefore in $\square OPS$, $\angle P = 90^\circ$ and $\angle O = 30^\circ$.

$$[OP] = [OS] \cos 30^\circ$$
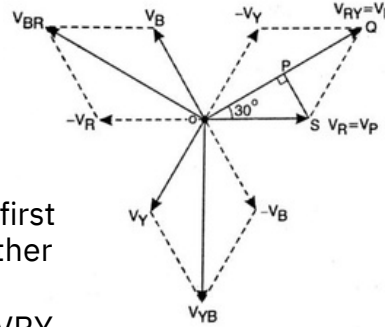
$$\text{Since } [OP] = V_L/2 \text{ and } [OS] = V_{ph}$$



2 marks for
phasor
diagram

3 marks for
stepwise
explanation

$$\frac{V_L}{2} = V_{ph} \cos 30^\circ$$

Thus **Line voltage = $\sqrt{3}$ (Phase Voltage)**

1 mark for
final answer

6 c) State the Thevenin's theorem. Also write stepwise procedure for applying

Thevenin's theorem to simple circuits.

Ans:

Thevenin's Theorem:

Any two terminal circuit having number of linear impedances and sources (voltage, current, dependent, independent) can be represented by a simple equivalent circuit consisting of a single voltage source V_{Th} in series with an impedance Z_{Th} ,

2 marks for
theorem

where the source voltage V_{Th} is equal to the open circuit voltage appearing across the two terminals due to internal sources of circuit and the series impedance Z_{Th} is equal to the impedance determined

while looking back into the circuit across the two terminals.
Step II: Calculation of V_{Th} : Remove R_L and find open circuit voltage across the load when the internal independent voltage sources are replaced by short-circuits and independent current sources by open circuits.

4 marks for

Step III: Calculation of R_{Th} : It is the resistance between the open circuited load terminals A & B while looking back into the network with all independent

Stepwise
procedure


voltage sources replaced by short-circuit & all independent current sources replaced by open circuits.
I: Identify the load branch (R_L): It is the branch whose current is to be

Model Answers
Winter – 2018 Examinations
Subject & Code: Electrical Circuits (22324)

replaced by open-circuit.

Step IV: Thevenin's equivalent circuit:

Thevenin Equivalent Circuit

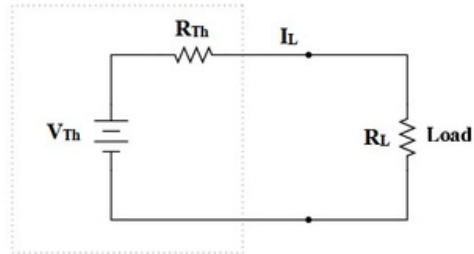

Step V: Determination of Load current:

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

21819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

22324

Instructions :

- (1) All Questions are compulsory.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

- | | Marks |
|---|-------|
| 1. Attempt any FIVE of the following : | 10 |
| (a) Draw power triangle for R-C series circuit. State the nature of power factor of this circuit. | |
| (b) Draw a phasor diagram for series R-L circuit showing supply voltage V, supply current I, voltage across resistor V_R & voltage across inductor V_L . | |
| (c) What is current magnification in parallel R-L-C circuit. | |
| (d) Define : Phase sequence and write equations for instantaneous values of 3-ph voltages. | |
| (e) Distinguish clearly between loop and mesh. | |
| (f) State Thevenin's theorem. | |
| (g) State Reciprocity theorem. | |
| 2. Attempt any THREE of the following : | 12 |
| (a) An AC series circuit consisting of $R = 15 \Omega$, $L = 0.1 \text{ H}$ and $C = 80 \mu\text{F}$ is supplied from 230 V, 50 Hz power supply. Determine : | |
| (i) Impedance of circuit | |
| (ii) Current drawn by the circuit | |
| (iii) Circuit power factor | |
| (iv) Reactive power drawn by circuit | |

- (b) An AC circuit consists of two branches in parallel.
 Branch I : $R = 10 \Omega$ and $L = 0.1 \text{ H}$ in series.
 Branch II : $C = 50 \mu\text{F}$.
 If the circuit is supplied from 200 V, 50 Hz supply, determine :
- Branch impedances.
 - Branch currents
 - Circuit power factor
 - Power consumed by the circuit
- (c) A star connected 3-ph load is supplied from 3-ph, 415 V, 50 Hz supply. If the line current is 20 A and total power taken from supply is 10 kW, then determine :
- Load resistance and reactance per phase.
 - Load power factor
 - Total 3-phase reactive power
- (d) Using Node analysis, find current I in the circuit shown in Fig. No. 1.

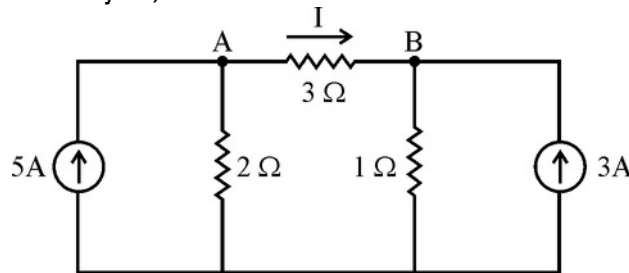


Fig. No. 1

3. Attempt any THREE of the following :
- A series R-L-C circuit consists of $R = 15 \Omega$, $L = 0.5 \text{ H}$ and $C = 25 \mu\text{F}$. If the circuit is supplied from 230 V, 50 Hz AC supply, determine :
 - Circuit power factor
 - Active power
 - Reactive power
 - Apparent power
 - Two parallel impedances $Z_1 = (10 + j8) \Omega$ and $Z_2 = (15 - j10) \Omega$ are connected to 230 V, 50 Hz AC supply. Using admittance method, calculate branch currents, total current and power factor of whole circuit.
 - Explain 'Neutral Shift' in case of 3-phase star-connected unbalanced load.
 - With neat circuit diagram, explain how to convert voltage source into current source and vice-versa.

- (e) Using Mesh analysis, find current I in the circuit shown in Fig. No. 2.


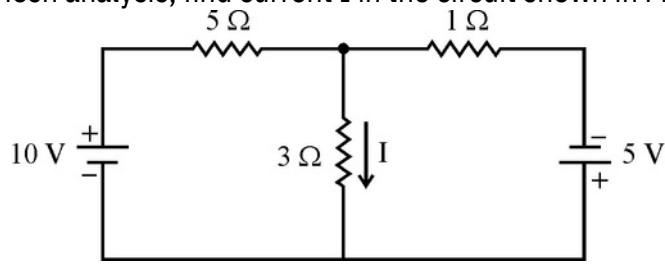



Fig. No. 2

4. Attempt any THREE of the following : 12
- (a) An inductive coil having resistance of 5Ω and inductance of 0.2 H is connected in series with a capacitor of $20 \mu\text{F}$. If this combination is connected to 230 V , variable frequency supply, determine :
- Resonant Frequency
 - Quality factor
 - Current at resonance
 - Voltage across inductive coil at resonance
- (b) R-C series combination having $R = 5 \Omega$ & $C = 20 \mu\text{F}$. If supply voltage is 110 V , 50 Hz , then
- Draw circuit diagram
 - Calculate branch currents using impedance method
 - Power absorbed by the coil
- (c) Three equal impedances having $R = 20 \Omega$ in series with $C = 50 \mu\text{F}$, are connected in delta across 415 V , 3-ph, 50 Hz AC supply. Determine :
- Impedance per phase
 - Phase and line currents
 - Total 3-ph power consumed by load
- (d) With neat circuit diagram, explain the concept of duality in Electric circuit.
State any four examples (pairs) of duality in electric circuit.
5. Attempt any TWO of the following : 12
- (a) An inductive coil having resistance of 10Ω and inductance of 0.5 H is connected in parallel with a capacitor of $50 \mu\text{F}$. Determine :
- Parallel resonant frequency
 - Quality factor of parallel circuit
 - Power consumed by circuit at resonance, if the supply voltage is 230 V .

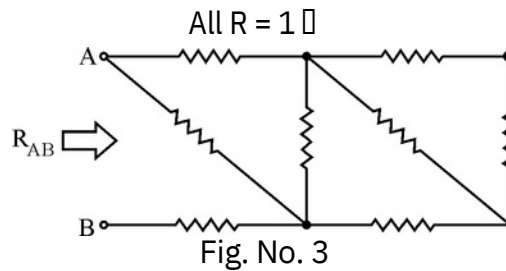- (b) Reduce the network shown in Fig. No. 3 by applying Star/Delta or Delta/Star transformation and determine equivalent resistance R_{AB} .




- (c) For network shown in Fig. No. 4, determine value of R so that maximum power is delivered to it. Also compute the maximum power delivered.

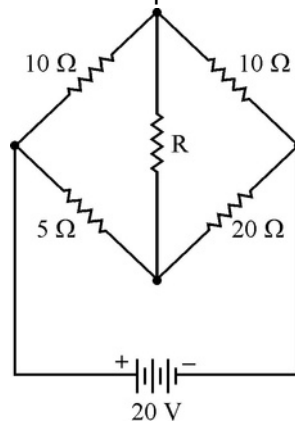

6. Attempt any TWO of the following :

12

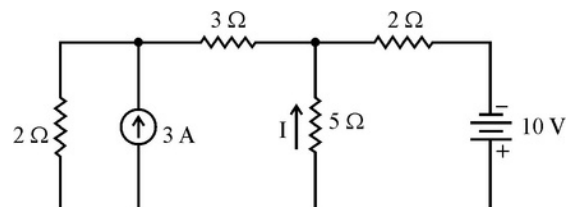- (a) A series RLC circuit consists of $R = 10 \Omega$, $L = 0.5 \text{ H}$ and $C = 20 \mu\text{F}$, is connected to 230 V, variable frequency supply. Determine :
- (i) Resonant frequency
 - (ii) Voltage magnification
 - (iii) Current drawn by circuit
 - (iv) Voltage across each element
 - (v) Power factor at resonance
 - (vi) The power consumed at resonance
- (b) Draw complete phasor diagram of voltages & currents for balanced delta-connected load, and prove the relationship between :
- (i) Line current & phase current
 - (ii) Line voltage & phase voltage
- (c) Apply superposition theorem to compute current I in the network shown in Fig. No. 5.



**Summer – 2019 Examinations
Model Answer
Subject & Code: ELECTRICAL CIRCUITS (22324)**

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner should assess understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner should give credit for any equivalent figure/figures drawn.
- 5) Credits to be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer (as long as the assumptions are not incorrect).
- 6) In case of some questions credit may be given by judgment on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept


**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

1 Attempt any FIVE of the following: 10

1 a) Draw power triangle for R-C series circuit. State the nature of power factor of this circuit.

Ans:

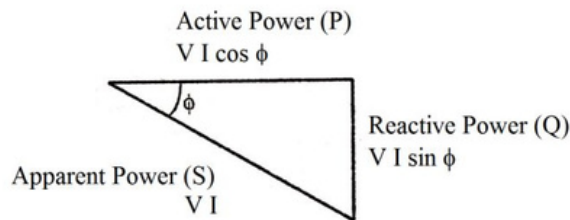


1 Mark for figure

Nature of Power-factor: **Leading**

1 Mark

1 b) Draw a phasor diagram for series R-L circuit showing supply voltage V, supply current I, voltage across resistor VR and voltage across inductor VL.

Ans –

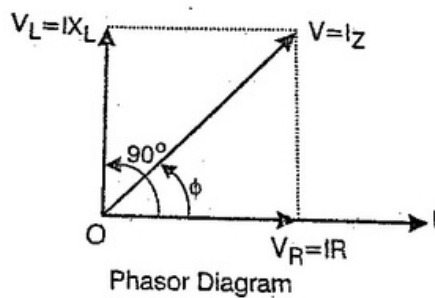

2 Marks for correct phasor diagram

1 c) What is current magnification in parallel R-L-C circuit?

Ans:

Current Magnification in Parallel R-L-C Circuit:

It is the ratio of current circulating between its branches to the line current drawn from the supply.

$$\text{Current magnification} = \frac{\text{Current through individual L or C branch}}{\text{Total Current}}$$

$$= \frac{I_L \text{ or } I_C}{I}$$

1 Mark for definition

OR

Current magnification in parallel resonant circuit is also known as Quality factor.

1 Mark for equation

$$Q \text{ factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

1 d) Define: Phase sequence and write equations for instantaneous value of 3-ph voltages.

Ans:

Phase sequence:


Phase sequence is defined as the order in which the voltages (or any other alternating quantity) of the three phases attain their positive maximum values.

In the following waveforms, it is seen that the R-phase voltage attains the positive maximum value first, and after angular distance of 120°, Y-phase voltage attains its positive maximum and further after 120°, B-phase voltage attains its positive maximum.

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

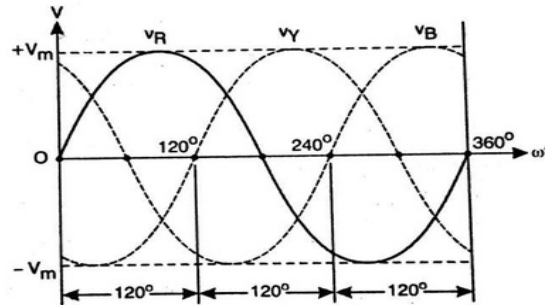attains its positive maximum value. So the phase sequence is R-Y-B.



Equations for instantaneous value of 3-ph voltages:

$$\begin{aligned} v_R &= V_m \sin(\omega t) \text{ volt} \\ v_Y &= V_m \sin(\omega t - 120^\circ) \text{ volt} \\ v_B &= V_m \sin(\omega t - 240^\circ) \text{ volt} \\ &= V_m \sin(\omega t + 120^\circ) \text{ volt} \end{aligned}$$

1 Mark for equations

1 e) Distinguish clearly between loop and mesh.

Ans:

Distinction between Loop & Mesh:

Sr. No.	Loop	Mesh
1	A loop is any closed path in a circuit, in which no node is other encountered more than once	A mesh is a loop that has no other loops inside of it
2	Every loop is not a mesh	Every mesh is a loop
3	Loops are used in a more general way for circuit analysis	Mesheres are used to analyze planar circuits

1 Mark for each of any two points = 2 Marks

1 f) State Thevenin's theorem.

Ans:

Thevenin's Theorem:

Any two terminal circuit having number of linear resistances and sources (voltage, current, dependent, independent) can be represented by a simple equivalent circuit consisting of a single voltage source V_{Th} in series with resistance R_{Th} , where the source voltage V_{Th} is equal to the open circuit voltage appearing across the two terminals due to internal sources of circuit and the series resistance R_{Th} is equal to the resistance of the circuit while looking back into the circuit across the two terminals, when the internal independent voltage sources are replaced by short-circuits and independent current sources by open circuits.

1 g) State Reciprocity theorem.

Ans:


Reciprocity theorem :

Reciprocity Theorem states that in any bilateral network if an **emf E or voltage source V** in one branch, say branch 'A' produces a **current I** in another branch, say branch 'B', then if the **emf E or voltage source**

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

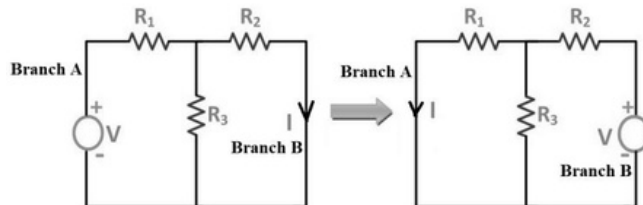V is moved from the branch A to the branch B, it will cause the same current I in the first branch 'A', where the emf has been replaced by a short circuit.



1 Mark for statement
1 Mark for circuit

2 Attempt any THREE of the following:

12

2 a) An AC series circuit consisting of $R = 15 \Omega$, $L = 0.1 \text{ H}$ and $C = 80 \mu\text{F}$ is supplied from 230V, 50Hz power supply. Determine:

- (i) Impedance of circuit
- (ii) Current drawn by the circuit
- (iii) Circuit power factor
- (iv) Reactive power drawn by circuit

Ans:

Data Given: $R = 15 \Omega$, $L = 0.1 \text{ H}$, $C = 80 \mu\text{F} = 80 \times 10^{-6}$,
 $V = 230\text{V}$, $f = 50\text{Hz}$

(i) Impedance of circuit (Z):

$$X_L = 2\pi fL$$

$$= 2 \times \pi \times 50 \times 0.1$$

$$\mathbf{X_L = 31.42 \Omega}$$

$$X_C = 1 / (2\pi fC)$$

$$= 1 / (2 \times \pi \times 50 \times 80 \times 10^{-6})$$

$$\mathbf{X_C = 39.79 \Omega}$$

$$Z = R + j(X_L - X_C) = 15 + j(31.4 - 39.79)$$

$$= \mathbf{15 - j8.4 = 17.19 \angle -29.24^\circ}$$

(ii) Current drawn by circuit:

$$I = \frac{V}{Z} = \frac{230 \angle 0^\circ}{17.19 \angle -29.24^\circ} = 13.37 \angle 29.24^\circ$$

(iii) Circuit Power factor:

$$\cos \phi = \frac{R}{Z} = \frac{15}{17.19} = \mathbf{0.87 \text{ (lead) OR}}$$

$$= \cos(29.24) = \mathbf{0.87 \text{ (lead)}}$$

(iv) Reactive power drawn by circuit:

$$P = VI \sin \phi = 230 \times 13.37 \times (0.48)$$

$$= \mathbf{1476.04 \text{ watt}}$$

1 Mark for each bit
= 4 Marks

2 b) An AC circuit consist of two branches in parallel.

Branch I: $R = 10 \Omega$ and $L = 0.1 \text{ H}$ in series

Branch II: $C = 50 \mu\text{F}$.

If the circuit is supplied from 200V, 50Hz supply, determine:

- (i) Branch impedances.
- (ii) Branch currents
- (iii) Circuit power factor
- (iv) Power consumed by the circuit.

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

Ans:

Data Given: Branch I: $R = 10 \Omega$ and $L = 0.1 \text{ H}$

Branch II: $C = 50 \mu\text{F} = 50 \times 10^{-6} \text{ F}$

$V = 200\text{V}$, $f = 50\text{Hz}$

(i) Branch impedances (Z_1 and Z_2):

Inductive reactance $X_L = 2\pi fL$

$$= 2 \times \pi \times 50 \times 0.1$$

$$\mathbf{X_L = 31.416 \Omega}$$

Capacitive reactance $X_C = 1 / (2\pi fC)$

$$X_C = 1 / (2\pi \times 50 \times 50 \times 10^{-6})$$

$$\mathbf{X_C = 63.66 \Omega}$$

Impedance $Z_1 = (10 + j31.416) \Omega = \mathbf{32.96 \angle 72.34^\circ \Omega}$

Impedance $Z_2 = 0 - j63.67 \Omega = \mathbf{63.67 \angle -90^\circ \Omega}$

(ii) Branch currents (I_1 and I_2):

Branch 1 current (I_1): $I_1 = V / Z_1 = 200 / 32.96 \angle 72.34^\circ$

$$\mathbf{I_1 = 6.06 \angle -72.34^\circ \text{ A} = (1.84 - j5.77) \text{ A}}$$

Branch 2 current (I_2): $I_2 = V / Z_2 = 200 / 63.67 \angle -90^\circ$

$$\mathbf{I_2 = 3.14 \angle 90^\circ \text{ A} = (0 + j3.14) \text{ A}}$$

Total Current (I): $I = I_1 + I_2 = (1.84 - j5.77) + (0 + j3.14)$

$$= 1.84 - j2.63 = 3.21 \angle -55.02^\circ \text{ A}$$

Angle between V and I is $\{0 - (-55.02)\} = 55.02^\circ$

(iii) Circuit power factor ($\cos \phi$):

$$\cos \phi = \cos(55.02^\circ) = \mathbf{0.573 \text{ lagging}}$$

(iv) Power consumed by the circuit:

$$P = V \times I \times \cos \phi = 200 \times 3.21 \times 0.573$$

$$\mathbf{P = 367.86 \text{ watt}}$$

1 Mark for
each bit
= 4 Marks

2 c) A star connected 3-ph load is supplied from 3-ph, 415V, 50Hz supply. If the line current is 20 A and total power taken from supply is 10 kW, then determine:

(i) Load resistance and reactance per phase.

(ii) Load power factor

(iii) Total 3-phase reactive power

Ans:

Data Given: $V_L = 415\text{V}$, $f = 50\text{Hz}$, $I_L = 20\text{A}$, $P = 10 \text{ kW} = 10000 \text{ W}$

In Star connection,

$$V_L = \sqrt{3} \times V_{Ph} \text{ and } I_L = I_{Ph}$$

$$\text{Therefore, } V_{Ph} = V_L / \sqrt{3} = 415 / \sqrt{3} = \mathbf{239.6 \text{ Volt.}}$$

$$\text{And } I_L = I_{Ph} = \mathbf{20 \text{ Amp.}}$$

$$\square \text{ Impedance per phase, } Z_{Ph} = V_{Ph} / I_{Ph} = 239.6 / 20$$

$$\mathbf{Z_{Ph} = 11.98 \Omega}$$

Total three-phase power is given by,

$$P = 3V_{Ph} I_{Ph} \cos \phi \quad \text{Or} \quad P = \sqrt{3} V_L I_L \cos \phi$$

$$10 \times 10^3 = 3 \times 239.6 \times 20 \times \cos \phi$$

Therefore,

$$\cos \phi = 10 \times 10^3 / (3 \times 239.6 \times 20)$$

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

$$\cos \phi = 0.695$$

$$\phi = \cos^{-1}(0.695) = 45.97^\circ$$

(i) Load Resistance and Reactance per phase:

$$\text{Resistance per phase (Rph)} = Z_{ph} \times \cos \phi = 11.98 \times 0.695$$

$$\mathbf{R_{ph} = 8.326 \Omega}$$

$$\text{Reactance per phase (Xph)} = Z_{ph} \times \sin \phi = 11.98 \times 0.718$$

$$\mathbf{X_{ph} = 8.601 \Omega}$$

(ii) Load Power Factor:

$$\cos \phi = 0.695 \text{ (lagging)}$$

(iii) Total 3-phase reactive power:

$$\text{Preactive} = \sqrt{3} \times V_L \times I_L \times \sin \phi = 3 V_{Ph} I_{Ph} \sin \phi$$

$$= \sqrt{3} \times 415 \times 20 \times \sin(45.97^\circ)$$

$$= 10336.01 \text{ VAR}$$

$$\mathbf{\text{Preactive} = 10.336 \text{ kVAR}}$$

1 Mark for

RPh

1 Mark for

XPh

1 Mark for

pf

1 Mark for

Reactive

power

2 d) Using Node analysis, find current I in the circuit shown in Fig. No. 1

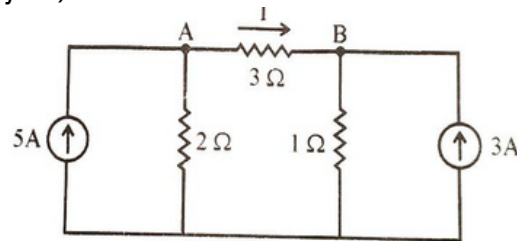


Fig. No. 1

Ans:

Apply KCL at node A

$$-5 + \frac{V_A}{2} + \frac{V_A - V_B}{3} = 0$$

$$V_A \left[\frac{1}{2} + \frac{1}{3} \right] - \frac{1}{3} V_B = 5$$

$$V_A [0.833] - V_B [0.33] = 5 \dots \dots \dots (1)$$

1 Mark for

Eq. (1)

Apply KCL at node B

$$\frac{V_B - V_A}{3} + \frac{V_B}{1} - 3 = 0$$

$$V_B \left[\frac{1}{3} + 1 \right] - V_A = 3$$

$$V_A [-0.33] + V_B [1.333] = 3 \dots \dots \dots (2)$$

1 Mark for

Eq. (2)

Expressing eq.(1) and (2) in matrix form,

$$\begin{bmatrix} 0.833 & -0.33 \\ -0.33 & 1.333 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 5 \\ 3 \end{bmatrix}$$

$$\therefore \Delta = \begin{vmatrix} 0.833 & -0.33 \\ -0.33 & 1.333 \end{vmatrix} = 1.1079 - 0.1089 = 0.999$$

By Cramer's rule,

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

$$V_A = \frac{5 - 0.33}{3 - 1.333} = \frac{(5 \times 1.333) - (3 \times 0.33)}{0.999} = \frac{6.665 - 0.99}{0.999} = 7.662 \text{ volt}$$

$$V_B = \frac{0.833 \times 5}{-0.333 - \Delta} = \frac{(0.833 \times 3) - (-0.33 \times 5)}{0.999} = \frac{2.499 + 1.65}{0.999} = 4.153 \text{ volt}$$

1 Mark for

V_A & V_B

1 Mark for I

Current through branch AB (3Ω) = $(V_A - V_B)/3 = (7.662 - 4.153)/3$
= 1.169 A from A to B

3 Attempt any FOUR of the following: 16

3 a) A series R-L-C circuit consists of $R = 15 \Omega$, $L = 0.5 \text{ H}$ and $C = 25 \mu\text{F}$. If the circuit is supplied from 230V, 50 Hz AC supply, determine:

- (i) Circuit power factor
- (ii) Active power
- (iii) Reactive power
- (iv) Apparent power

Ans:
Data Given: $R = 15 \Omega$, $L = 0.5 \text{ H}$, $C = 25 \mu\text{F} = 25 \times 10^{-6} \text{ F}$
 $V = 230 \text{ V}$, $f = 50 \text{ Hz}$

(i) Circuit power factor:

$$X_L = 2\pi fL = 2 \times \pi \times 50 \times 0.5 = 157.08 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times \pi \times 50 \times 25 \times 10^{-6}} = 127.32 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{15^2 + (157.08 - 127.32)^2}$$

$$= 33.326 \Omega$$

1 Mark for

each bit

= 4 Marks

$$\text{Circuit power factor } \cos \phi = \frac{R}{Z} = \frac{15}{33.326} = \mathbf{0.45 \text{ (lagging)}}$$

$$\text{Power factor angle } \phi = \cos^{-1}(0.45) = 63.25^\circ$$

(ii) Active Power (P):

$$\text{Circuit current } I = \frac{V}{Z} = \frac{230}{33.326} = 6.901 \text{ A}$$

$$P = VI \cos \phi = 230 \times 6.901 \times 0.45$$

$$= \mathbf{714.25 \text{ W}}$$

(iii) Reactive Power (Q):

$$Q = VI \sin \phi = 230 \times 6.901 \times \sin(63.25^\circ)$$

$$= \mathbf{1417.36 \text{ VAR}}$$

(iv) Apparent Power (S):

$$\text{Apparent Power} = S = VI = 230 \times 6.901 = \mathbf{1587.23 \text{ VA}}$$

3 b) Two parallel impedances $Z_1 = (10 + j8) \Omega$ and $Z_2 = (15 - j10) \Omega$ are connected to 230V, 50 Hz AC supply. Using admittance method, calculate branch currents, total current and power factor of whole circuit.

Ans:

Data Given: $Z_1 = (10 + j8) \Omega = 12.806 \angle 38.66^\circ \Omega$
 $Z_2 = (15 - j10) \Omega = 18.03 \angle -33.69^\circ \Omega$
 $V = 230 \angle 0^\circ \text{ V}$, $f = 50 \text{ Hz}$

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

$$Y_1 = \frac{1}{Z_1} = \frac{1}{12.806 \angle 38.66^\circ} = 0.078 \angle -38.66^\circ \text{ } \cup = (0.06 - j0.049) \cup$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{18.03 \angle -33.69^\circ} = 0.055 \angle 33.69^\circ \text{ } \cup = (0.046 + j0.031) \cup$$

$$Y = Y_1 + Y_2 = G + jB = 0.06 - j0.049 + 0.046 + j0.031 = 0.106 - j0.018 = 0.1075 \angle -9.64^\circ \cup$$

1 Mark for
each bit
= 4 Marks

(i) Current I₁ flowing through admittance Y₁:

$$= V \times Y_1 = (230 \angle 0^\circ) \times (0.078 \angle -38.66^\circ)$$

$$I_1 = 17.94 \angle -38.66^\circ \text{ A} = (14 - j 11.21) \text{ A}$$

(ii) Current I₂ flowing through admittance Y₂:

$$= V \times Y_2 = (230 \angle 0^\circ) \times (0.055 \angle 33.69^\circ)$$

$$I_2 = 12.65 \angle 33.69^\circ \text{ A} = (10.53 + j 7.02) \text{ A}$$

(iii) Total Current (I):

$$I = V \times Y = (230 \angle 0^\circ) \times (0.1075 \angle -9.64^\circ) = \mathbf{24.725 \angle -9.64^\circ \text{ A}}$$

OR

$$I = I_1 + I_2 = (14 - j 11.21) + (10.53 + j 7.02)$$

$$= (24.53 - j 4.19) = \mathbf{24.89 \angle -9.69^\circ \text{ A}}$$

(iv) Power factor (cos φ)

$$\phi = \text{voltage ref. angle} - \text{current angle} = 0 - (-9.64^\circ) = 9.64$$

$$\text{Therefore, Power factor} = \cos(9.64) = \mathbf{0.986 \text{ (lagging)}}$$

3 c) Explain 'Neutral Shift' in case of 3-phase star-connected unbalanced load.

Ans:

Neutral Shift:



1 Mark for
phasor
diagram

Electrically "Neutral" means no resultant charge or zero potential condition.

When three impedances are connected in star, there is a common point "O" where one end of each impedance is connected. This common point is called star point. Other remaining ends are connected to the three-phase supply terminals, as shown above.

3 Marks for

When the three-phase supply voltage is balanced and three impedances Z_a , Z_b and Z_c are identical i.e $Z_a = Z_b = Z_c = Z$, then all the three impedances carry equal currents but displaced from each other by 120° . Thus currents are balanced, phase voltages are also balanced and the star point "O" is held at zero potential. Even if this point "O" is not connected to neutral, its potential is zero. Therefore, this point is referred as neutral. In other words we can say that under balanced condition (i.e when both supply voltage and load are balanced), the neutral point appears at physical common or star point "O".

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

When the three-phase supply voltage is balanced but three impedances Z_a , Z_b and Z_c are not identical i.e $Z_a \neq Z_b \neq Z_c$, then the three impedances carry unequal currents. Thus currents are unbalanced, phase voltages then get unbalanced and the star point “O” can not be maintained at zero potential, rather it has some nonzero potential. Therefore, this point “O” can not be now referred as neutral. However, it is observed that there is some another point O’ at which the potential is zero. So this point O’ is now referred as neutral. In other words we can say that under unbalanced condition, the neutral point get shifted from star point “O” to some other point O’, as shown in the phasor diagram. This is referred as “Neutral Shift”.

- 3 d) With neat circuit diagram, explain how to convert voltage source into current source and vice-versa.

Ans:


Conversion of voltage source into equivalent current source & vice-versa:

Let V_S be the practical voltage source magnitude and

Z_V be the internal series impedance of the voltage source.

I_S be the equivalent current source magnitude and

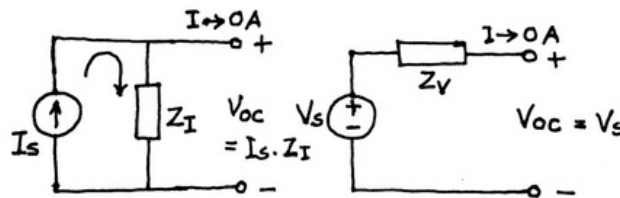Z_I be the internal parallel impedance of current source.




1 mark

The open circuit terminal voltage of voltage source is $V_{OC} = V_S$

The open circuit terminal voltage of current source is $V_{OC} = I_S \square Z_I$

Therefore, we get $V_S = I_S \square Z_I$ (1)

½ mark

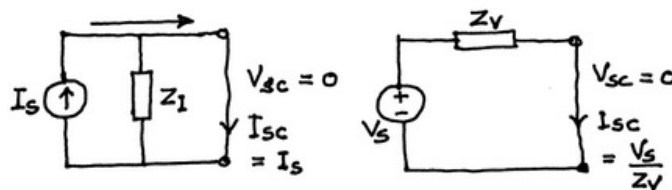

1 mark

The short circuit output current of voltage source is $I_{SC} = V_S / Z_V$

The short circuit output current of current source is $I_{SC} = I_S$

Therefore, we get $I_S = V_S / Z_V$ (2)

Therefore, we get $V_S = I_S \square Z_V$(3)

½ mark

On comparing eq. (1) and (3), it is clear that $Z_I = Z_V = Z$ (4)

½ mark

Thus the internal impedance of both the sources is same, and the magnitudes of the source voltage and current are related by Ohm’s law,

$$V_S = I_S \square Z$$

½ mark

- 3 e) Using mesh analysis, find current I in the circuit shown in Fig No.2

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)


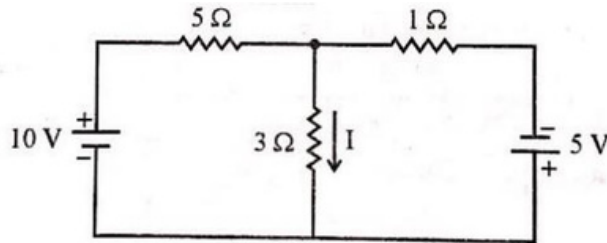


Fig. No. 2

Ans:

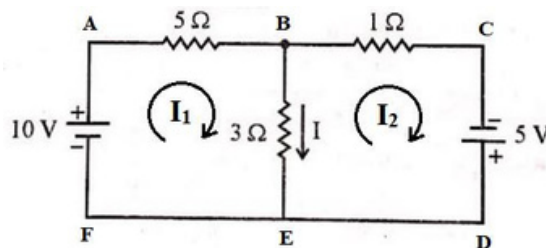

By applying KVL to loop ABEFA

$$10 - 5I_1 - 3(I_1 - I_2) = 0 \quad (1)$$

By applying KVL to Loop DCBED

$$-3I_1 + 4I_2 = 5 \quad (2)$$

Expressing eq.(1) and (2) in matrix form, $\begin{pmatrix} 8 & -3 \\ -3 & 4 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 10 \\ 5 \end{pmatrix}$

$$\therefore \Delta = \begin{vmatrix} 8 & -3 \\ -3 & 4 \end{vmatrix} = 32 - (9) = 23$$

By Cramer's rule,

$$I_1 = \frac{\begin{vmatrix} 10 & -3 \\ 5 & 4 \end{vmatrix}}{\Delta} = \frac{(10 \times 4) - (5 \times -3)}{23} = \frac{40 + 15}{23} = 2.39 \text{ A}$$

$$I_2 = -3 \frac{\begin{vmatrix} 8 & 10 \\ -3 & 5 \end{vmatrix}}{\Delta} = \frac{(8 \times 5) - (-1 \times 0 \times -3)}{23} = \frac{40 + 30}{23} = 3.043 \text{ A}$$

**Current flowing through resistance of 3Ω = (I₂ - I₁) = (3.043 - 2.39)
= 0.653 A from E to B
= -0.653A from B to E**

1 Mark for
Eq. 1

1 Mark for
Eq. 2

½ Mark

½ Mark

1 Mark

4 Attempt any THREE of the following:

12

4 a) An inductive coil having resistance of 5Ω and inductance of 0.2 H is connected in series with a capacitor of 20μF. If this combination is connected to 230 V, variable frequency supply, determine:

- (i) Resonant frequency
- (ii) Quality factor
- (iii) Current at resonance
- (iv) Voltage across inductive coil at resonance.

Ans:

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

Data Given: $R = 5\Omega$, $L = 0.2\text{ H}$, $C = 20\ \mu\text{F} = 20 \times 10^{-6}\text{ F}$, $V = 230\text{ V}$

i) Resonant Frequency:

$$\text{Resonant frequency} = f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \times 3.142 \sqrt{0.2 \times 20 \times 10^{-6}}} = \mathbf{79.58\text{ Hz}} \quad \text{1 Mark}$$

ii) Quality factor:

$$Q \text{ factor} = \frac{1}{R} \sqrt{L/C}$$

$$Q \text{ factor} = \frac{1}{5} \sqrt{0.2 / (20 \times 10^{-6})} = \mathbf{20} \quad \text{1 Mark}$$

iii) Current:

At resonance $R = Z$
 \therefore Current $I = V/Z = 230/5 = \mathbf{46\text{ A}}$ 1 Mark

iv) Voltage across inductive coil at resonance:

Inductive reactance of coil at resonance $X_L = 2\pi f_r L$
 $X_L = 2\pi(79.58)(0.2) = 100\ \Omega$
 Impedance of inductive coil at resonance, $Z = R + jX_L$
 $Z = 5 + j100 = 100.125 \angle 87.14^\circ$
 Voltage across inductive coil at resonance, 1 Mark
 $V_L = I Z = 46(100.125) = \mathbf{4605.75\text{ volt}}$


4 b) A coil having resistance of $10\ \Omega$ and inductance of 0.15 H is connected in parallel with R-C series combination having $R = 5\ \Omega$ and $C = 20\ \mu\text{F}$. If supply voltage is 110 V , 50 Hz , then

- (i) Draw circuit diagram
- (ii) Calculate branch currents using impedance method
- (iii) Power absorbed by the coil

Ans:

Data Given: $R_L = 10\ \Omega$, $L = 0.15\text{ H}$, $R_C = 5\ \Omega$, $C = 20\ \mu\text{F} = 20 \times 10^{-6}\text{ F}$
 $V = 110\ \text{V}$, $f = 50\text{ Hz}$

Circuit Diagram:

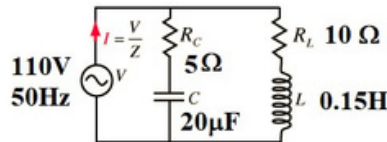

1 Mark for
circuit
diagram

Branch Currents:

Inductive reactance, $X_L = 2\pi f L = 2\pi \times 50 \times 0.15 = 47.124\ \Omega$

Capacitive reactance, $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 20 \times 10^{-6}} = 159.155\ \Omega$

Impedance of inductive coil,

$$Z_L = R_L + jX_L = 10 + j47.124 = 48.17 \angle 78.02^\circ\ \Omega$$

Impedance of R-C series combination,

$$Z_C = R_C - jX_C = 5 - j159.155 = 159.23 \angle -88.20^\circ\ \Omega$$

Inductive coil current is given by,

$$I_L = \frac{V}{Z_L} = \frac{110 \angle 0^\circ}{48.17 \angle 78.02^\circ} = \mathbf{2.28 \angle -78.02^\circ\text{ A}} = \mathbf{(0.47 - j2.23)\text{ A}}$$

1 Mark for
IL

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

Capacitive branch current is given by,

$$I_C = \frac{V}{\sqrt{159.23^2 - 88.20^2}} = \mathbf{0.69 \angle 88.20^\circ \text{ A} = (0.0217 + j0.69) \text{ A}}$$

1 Mark for IC
1 Mark for Pcoil

Power absorbed by the coil:

$$P_{\text{coil}} = V \times I_L \times \cos \phi = 110 \times 2.28 \times \cos(78.02) = \mathbf{52.06 \text{ W}}$$

$$= (I_L)^2 R_L = (2.28)^2 (10) = \mathbf{51.984 \text{ watt}}$$

(NOTE: Examiner is requested to ignore the round-off errors)

- 4 c) Three equal impedances having $R = 20 \Omega$ in series with $C = 50 \mu\text{F}$ are connected in delta across 415 V, 3-ph, 50 Hz AC supply. Determine:
- Impedance per phase
 - Phase and line currents
 - Total 3-ph power consumed by load

Ans:

Data Given: $R_{\text{ph}} = 20 \Omega$, $C = 50 \mu\text{F} = 50 \times 10^{-6} \text{ F}$, $V_L = 415 \text{ V}$, $f = 50 \text{ Hz}$

$$X_C \text{ per phase} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} = \mathbf{63.66 \Omega}$$

½ Mark

$$\square \text{ Impedance per phase, } Z_{\text{ph}} = \sqrt{R_{\text{ph}}^2 + X_C^2} = \sqrt{20^2 + 63.66^2} = \mathbf{66.73 \Omega}$$

1 Mark

For delta connected load

$$\text{Phase voltage} = V_{\text{ph}} = V_L = 415 \text{ V}$$

$$\text{Phase current, } I_{\text{ph}} = \frac{V_{\text{ph}}}{Z_{\text{ph}}} = \frac{415}{66.73} = \mathbf{6.22 \text{ A}}$$

½ Mark for I_{ph}

$$\text{Line current, } I_L = \sqrt{3} \times I_{\text{ph}} = \sqrt{3} \times 6.22 = \mathbf{10.77 \text{ A}}$$

1 Mark for I_L

$$\text{Load power factor, } \cos \phi = \frac{R_{\text{ph}}}{Z_{\text{ph}}} = \frac{20}{66.73} = 0.2997 \text{ (leading)}$$

Total 3-ph Power consumed by load,

1 Mark

$$P_{3\phi} = \sqrt{3} \times V_L \times I_L \times \cos \phi = \sqrt{3} \times 415 \times 10.77 \times 0.2997 = \mathbf{2320.12 \text{ W}}$$

OR

$$= 3 \times V_{\text{ph}} \times I_{\text{ph}} \times \cos \phi = 3 \times 415 \times 6.22 \times 0.2997 = \mathbf{2320.85 \text{ W}}$$

(NOTE: Examiner is requested to ignore the round-off errors)

- 4 d) With neat circuit diagram, explain the concept of duality in electric circuit.

State any four examples (pairs) of duality in electric circuit.

Ans:

Concept of duality:

When the two circuit elements are represented by mathematical equations of similar nature, then these elements are called dual elements of each other.

Examples:

(i) A resistance is represented by mathematical equation based on Ohm's law as, $R = V/I$ and the conductance is represented by $G = I/V$.

(ii) A voltage across an inductance is represented by $v = L \frac{di}{dt}$ and the current

through a capacitor is represented by $i = \frac{dv}{dt} C$

On comparing the above equations we can form pairs of dual elements or quantities:

$$\begin{aligned} \text{Resistance } R &\leftrightarrow \text{Conductance } G \\ \text{Inductance } L &\leftrightarrow \text{Capacitance } C \\ \text{Voltage } v &\leftrightarrow \text{Current } i \end{aligned}$$

**Summer – 2019 Examinations
Model Answer**


Subject & Code: ELECTRICAL CIRCUITS (22324)

Similarly, we can apply this concept to electric circuits and say that when the two circuits are represented by similar mathematical equations, then such circuits are called dual circuits of each other. Consider a series R-L-C circuit, the voltage equation can be written 1 Mark

$$v(t) = R.i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt \dots\dots\dots(1)$$

Consider a parallel R-L-C circuit, the current equation can be written as:
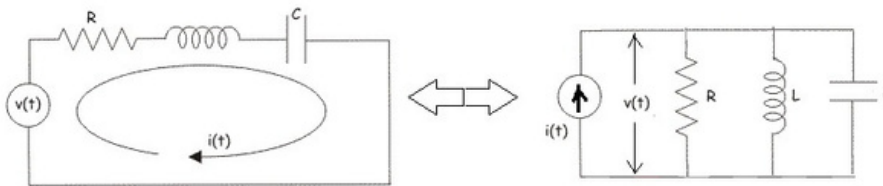
$$i(t) = \frac{1}{R}v(t) + C \frac{dv(t)}{dt} + \frac{1}{L} \int v(t) dt \dots\dots\dots(2)$$



1 Mark

On comparing equations (1) & (2), it is seen that both the equations are integro-differential equations of similar kind. Therefore, the two circuits are dual circuits. The dual element pairs are:

- Voltage source $v(t) \leftrightarrow$ Current source $i(t)$
- Resistance $(R) \leftrightarrow$ Conductance $(G = 1/R)$
- Inductance $(L) \leftrightarrow$ Capacitance (C)
- Series Circuit \leftrightarrow Parallel circuit

Examples of duality in electric circuit

- voltage – current
- parallel circuit – series circuit
- resistance – conductance
- voltage division – current division
- impedance – admittance
- capacitance – inductance
- reactance – susceptance
- short circuit – open circuit
- Kirchhoff's Voltage law – Kirchhoff's Current law
- Mesh – Node
- Thevenin's theorem – Norton's theorem

1 Mark for any four pairs

5 Attempt any TWO of the following:

12

- 5 a) An inductive coil having resistance of 10Ω and inductance of 0.5 H is connected in parallel with a capacitor of $50 \mu\text{F}$. Determine:
- (i) Parallel resonant frequency.
 - (ii) Quality factor of parallel circuit
 - (iii) Power consumed by circuit at resonance, if the supply voltage is 230V .

Ans:

Data Given:

$$R = 10 \Omega, \quad L = 0.5 \text{ H}, \quad C = 50 \mu\text{F}, \quad V = 230\text{V}$$

- i) Parallel resonant frequency**

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad 1 \text{ Mark}$$

$$= \frac{1}{2\pi} \sqrt{\frac{1}{0.5 \times 50 \times 10^{-6}} - \frac{10^2}{0.5^2}} \quad 1 \text{ Mark}$$

= 31.67 Hz

ii) Quality factor of parallel circuit

$$Q \text{ factor} = \frac{2\pi L f_r}{R} \quad 1 \text{ Mark}$$

$$= \frac{2\pi \times 0.5 \times 31.67}{10}$$

= 9.949 1 Mark

iii) Power consumed by circuit at resonance:


Reactance of coil = $X_L = 2\pi f_r L = 2\pi(31.67)(0.5) = 99.49\Omega$ 1 Mark

Impedance of coil = $Z = R + jX_L = (10 + j99.49) = 99.99\angle 84.26^\circ\Omega$ 1 Mark

Current flowing through the coil $I = V/Z = 230/99.99 = 2.3A$ 1 Mark


Power consumed by circuit at resonance = Power consumed by coil resistance = $I^2 R = (2.3)^2(10) = 52.9 W$ 1 Mark

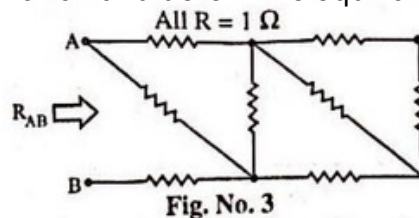5 b) Reduce the network shown in Fig. No. 3 by applying Star/Delta or Delta/Star transformation and determine equivalent resistance R_{AB} .



Ans:

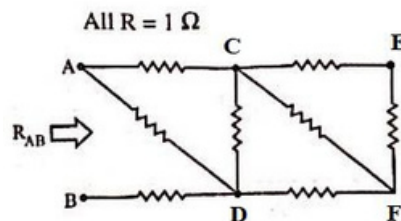(NOTE: This problem can be solved without using Star/Delta or Delta/Star transformations. However, since it is asked to use the transformation, the marks are awarded only if student has solved this problem using at least one Star/Delta or Delta/Star transformation)



The resistance R_{CE} and R_{EF} are in series.

$$R_{CF1} = 1 + 1 = 2$$

There is another path from C to F directly through R_{CF2}

$$R_{CF2} = 1$$

Since the two paths from C to F are in parallel,

$$R_{CF} = R_{CF1} \parallel R_{CF2} = 2 \parallel 1 = (2)(1)/(2+1) = 2/3 \approx 0.667$$

This R_{CF} appears in series with R_{FD}

$$R_{CD1} = R_{CF} + R_{DF} = 0.667 + 1 = 1.667$$

**Summer – 2019 Examinations
Model Answer**


Subject & Code: ELECTRICAL CIRCUITS (22324)

There is another path from C to D directly through 1Ω .

$$R_{CD2} = 1 \Omega$$

Since the two paths from C to D are in parallel,
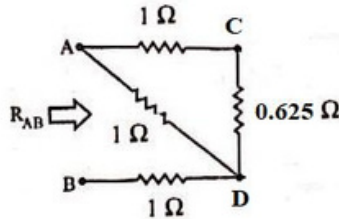
$$R_{CD} = R_{CD1} \parallel R_{CD2} = 1.667 \parallel 1 = (1.667)(1)/(1.667+1) = 1.667/2.667 = 0.625 \Omega$$



2 Marks

Converting Delta ACD into equivalent Star,

$$R_C = (R_{AC} \cdot R_{CD}) / (R_{AC} + R_{CD} + R_{DA}) = (1)(0.625) / (1 + 0.625 + 1) = 0.625 / 2.625$$


$$\mathbf{R_C = 0.238 \Omega}$$

$$R_A = (R_{AC} \cdot R_{DA}) / (R_{AC} + R_{CD} + R_{DA}) = (1)(1) / (1 + 0.625 + 1) = 1 / 2.625$$

$$\mathbf{R_A = 0.38 \Omega}$$

$$R_D = (R_{CD} \cdot R_{DA}) / (R_{AC} + R_{CD} + R_{DA}) = (0.625)(1) / (1 + 0.625 + 1) = 0.625 / 2.625$$

$$\mathbf{R_D = 0.238 \Omega}$$

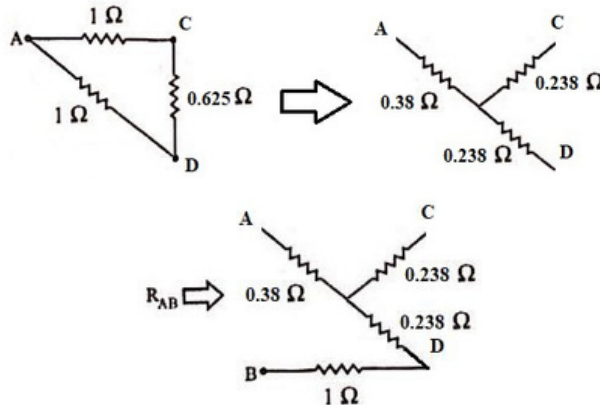

3 Marks

$$R_{AB} = R_A + R_D + R_{DB} = 0.38 + 0.238 + 1 = 1.618 \Omega$$

$$\mathbf{R_{AB} = 1.618 \Omega}$$

1 Mark

- 5 c) For network shown in Fig. No. 4, determine value of R so that maximum power is delivered to it. Also compute the maximum power delivered.

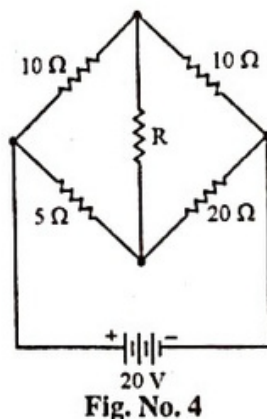


Fig. No. 4

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)



Ans: According to the maximum power transfer theorem, the maximum power will be transferred to the resistance R only when the value of R is equal to

the Thevenin equivalent resistance R_{Th} of the remaining circuit seen between the open-circuited terminals of the resistance R with all internal

independent sources replaced by their respective internal resistances,

i.e

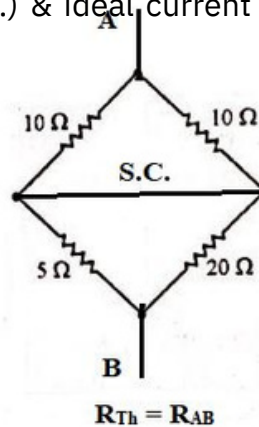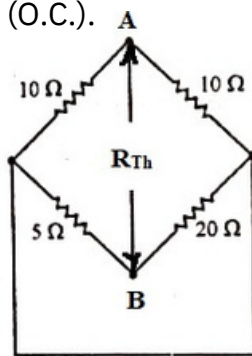ideal voltage source by short-circuit (S.C.) & ideal current source by open-circuit (O.C.).



From the simplified circuit, we can write,

$$R_{Th} = (10 \parallel 10) + (5 \parallel 20) = (100/20) + (100/25) = 5 + 4 = 9 \Omega$$

2 Marks

□ For maximum power transfer $R = R_{Th} = 9 \Omega$ □


Computation of Maximum power delivered:

The current that can flow through R can be determined by using Thevenin

theorem. The circuit excluding R can be represented by simple

Thevenin

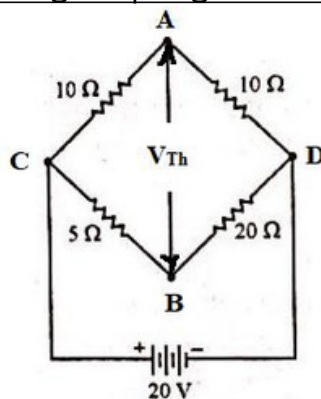equivalent circuit consisting of a voltage source (V_{Th}) in series with resistance R_{Th} .



Current flowing through path CAD: $I_1 = 20/(10+10) = 20/20 = 1A$
 Current flowing through path CBD: $I_2 = 20/(5+20) = 20/25 = 0.8A$
 Voltage between terminals A & D: $V_{AD} = I_1 (10) = 1(10) = 10V$
 Voltage between terminals B & D: $V_{BD} = I_2 (20) = 0.8(20) = 16V$
 It is seen that potential of A is 10V above that of D and potential of B is 16V above that of D. Therefore, point B is at higher potential

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

than A by 6V. i.e $V_{Th} = V_{BA} = V_{BD} - V_{AD} = 16 - 10 = 6V$

$$\boxed{V_{Th} = 6V}$$


1 Mark for V_{Th}

B) Determination of Thevenin equivalent resistance (R_{Th}):

It is already computed above..

$$\boxed{R_{Th} = 9 \Omega}$$

C) Thevenin equivalent circuit :

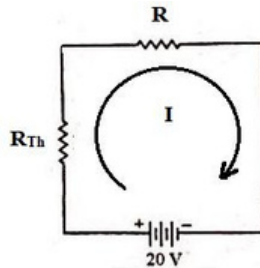

2 Marks for Thevenin eq. circuit

$$\text{Circuit current } I = V / (R_{Th} + R) = 20 / (9 + 9) = 20 / 18 = 1.11A$$

$$\text{Maximum Power delivered to } R = P_{R_{max}} = I^2 R$$

$$= (1.11)^2 (9) = 11.09 \text{ watt}$$

1 Mark for max. power

6 Attempt any TWO of the following:

12

6 a) A series RLC circuit consists of $R = 10 \Omega$, $L = 0.5 \text{ H}$ and $C = 20 \mu\text{F}$ is connected to 230V, variable frequency supply. Determine:

- (i) Resonant frequency
- (ii) Voltage magnification
- (iii) Current drawn by the circuit
- (iv) Voltage across each element
- (v) Power factor at resonance
- (vi) The power consumed at resonance.

Ans: Resonant Frequency:

i)

$$\text{Resonant frequency } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore f_r = \frac{1}{2\pi\sqrt{(0.5 \times 20 \times 10^{-6})}} = 50.33 \text{ Hz}$$

1 Mark for each bit = 6 Marks

ii) **Voltage Magnification:**

$$\begin{aligned} \text{Q factor} &= \frac{1}{R} \sqrt{\frac{L}{C}} \\ &= \frac{1}{10} \sqrt{\frac{0.5}{20 \times 10^{-6}}} \\ &= 15.81 \end{aligned}$$

iii) **Current drawn by the circuit:**

At resonance $R = Z$

$$\therefore \text{Current } I = \frac{V}{Z} = \frac{230}{10} = 23 \text{ A}$$

iv) **Voltage across each element:**

$$V_R = I.R = 23 \times 10 = 230V$$

$$V_L = I.X_L = I \times 2\pi f_r L = 23 \times 2\pi \times 50.33 \times 0.5 = 3636.68V$$

$$V_C = I.X_C = I \times 1 / (2\pi f_r C)$$

$$= 23 \times 1 / (2\pi \times 50.33 \times 20 \times 10^{-6}) = 3636.56V$$

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

v) **Power factor at resonance**

vi) At Resonance p.f = 1

Power at resonance:



At Resonance p.f = 1

$$\therefore P = V \times I = 230 \times 23 = 5290 \text{ W}$$

6 b) Draw complete phasor diagram of voltages & currents for balanced delta-connected load and prove the relation between:

- (i) Line current and Phase current
- (ii) Line voltage and Phase voltage

Ans:

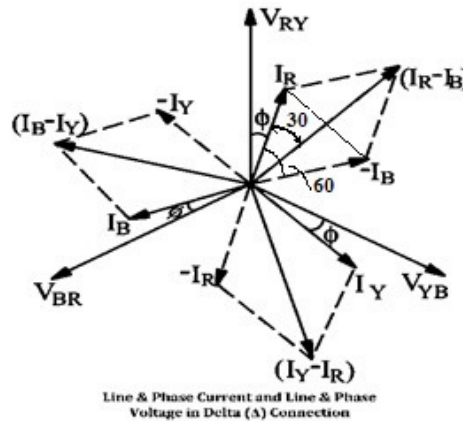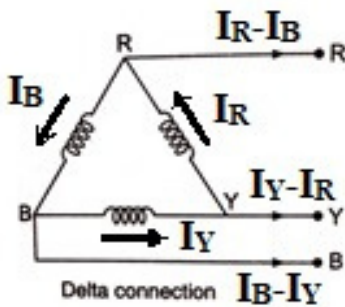

1 Mark for
circuit
diagram

2 Marks for
Phasor
diagram

(i) Line current and Phase current:

From above diagram current in each lines are vector difference of the two phase currents flowing through that line.

For example:

$$\text{Current in line R is } IL1 = IR - IB$$

$$\text{Current in line Y is } IL2 = IY - IR$$

$$\text{Current in line B is } IL3 = IB - IY$$

Current in line R is found by compounding IR and IB and value given by parallelogram in phasor diagram.

Angle between IR and IB is 60° ,

where $|IR| = |IB| = \text{Phase current } I_{ph}$

$$I_{L1} = IR - I_B = 2I_{ph} \cos\left(\frac{60^\circ}{2}\right) = 2I_{ph} \frac{\sqrt{3}}{2} = \sqrt{3}I_{ph}$$

$$I_{L2} = IY - I_R = 2I_{ph} \cos\left(\frac{60^\circ}{2}\right) = 2I_{ph} \frac{\sqrt{3}}{2} = \sqrt{3}I_{ph}$$

$$I_{L3} = IB - I_Y = 2I_{ph} \cos\left(\frac{60^\circ}{2}\right) = 2I_{ph} \frac{\sqrt{3}}{2} = \sqrt{3}I_{ph}$$

$$\text{As } IL1 = IL2 = IL3 = I_L$$

$$\mathbf{IL} = \sqrt{3}I_{ph}$$

M marks for
stepwise
derivation of
current
relationship

(ii) Line Voltage and Phase voltage:

From circuit diagram, it is clear that:

Voltage across Phase R (winding connected between terminals R & Y)

**Summer – 2019 Examinations
Model Answer**

Subject & Code: ELECTRICAL CIRCUITS (22324)

= Voltage between lines R & Y = VL = Line voltage

□ **Phase Voltage = Line Voltage**

□ **VPh = VL**

1 Mark for
voltage
relationship

- 6 c) Apply superposition theorem to compute current I in the network shown in Fig. No. 5.


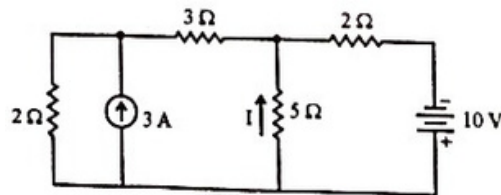


Fig. No. 5

Ans:

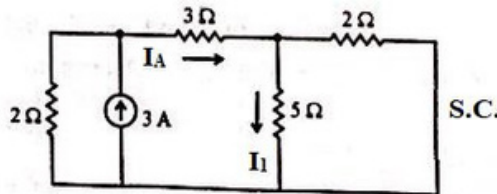(A) Consider current source of 3A acting alone:

The 10V source is replaced by short-circuit (S.C.)



½ Mark for
figure

The total resistance appearing across 2Ω (or current source) is given by,

$$= 3 + \{5 \parallel 2\} = 3 + (10/7) = 31/7 = 4.43 \Omega$$

The current $I_A = 3 \times \{2 / (2 + 4.43)\} = 0.933 \text{ A}$

The current through 5Ω due to 3A source alone is given by current division formula as,


$$I_1 = I_A (2) / (2 + 5) = 0.933 (2/7) = \mathbf{0.2666 \text{ A (downward)}}$$

1 Mark for
 I_A

1 Mark for I_1

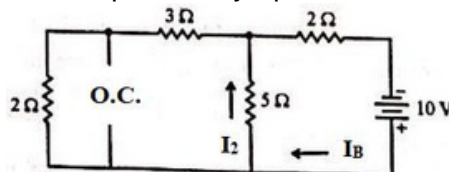(B) Consider voltage source of 10V acting alone:

The 3A source is replaced by open-circuit (O.C.)



½ Mark for
figure

The total resistance appearing across 5Ω is given by,

$$= 3 + 2 = 5 \Omega$$

The total resistance appearing across 10V source is,

$$R = 2 + (5 \parallel 5) = 2 + (25/10) = 2 + 2.5 = 4.5 \Omega$$

The current $I_B = V/R = 10/4.5 = 2.22 \text{ A}$

The current through 5Ω due to 10V source alone is given by,

$$I_2 = I_B (5) / (5 + 5) = 2.22 (0.5) = \mathbf{1.11 \text{ A (upward)}}$$

1 Mark for
 I_B

1 Mark for I_2

By Superposition theorem, the upward current through 5Ω due to both 1 mark for I sources is given by,

$$\mathbf{I = -I_1 + I_2 = (-0.2666 + 1.11) = 0.8434 \text{ A}}$$

11920
3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

22324

Instructions :

- (1) All Questions are compulsory.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following : 10
- (a) Define Conductance and Susceptance related to AC circuit and state their units.
 - (b) Draw power triangle for R-L series circuit. Write equation of power in rectangular form.
 - (c) Express an instantaneous value of an alternating current varying sinusoidally in terms of its maximum value, frequency and time.
 - (d) State relationship between line and phase values of voltage and current in balanced delta connection.
 - (e) Distinguish clearly between loop and mesh.
 - (f) State the value of internal resistance of (i) Ideal Voltage Source and (ii) Ideal Current Source.
 - (g) State Norton's Theorem.

2. Attempt any THREE of the following : 12
- (a) With neat diagram, explain the phasor representation of sinusoidal quantity. For
 - (b) a parallel circuit consisting of an inductive branch (RL) in parallel with a capacitive branch (RC), draw phasor diagram and derive equation for resonant frequency. With the help of neat phasor diagram, derive the relationship
 - (c) between line and phase values of voltage in balanced star connection. State the equivalent delta connection for star connection of three resistances
 - (d) R_1, R_2 & R_2 , with proper equations.
3. Attempt any THREE of the following : 12
- (a) For series R-L-C circuit, draw neat circuit diagram. State the conditions for RLC series ckt. Draw phasor diagram and voltage triangle impedance triangle for any 1 condition. State any four properties of Parallel Resonance. With neat labelled
 - (b) diagram, explain unbalanced star connected load.
 - (c)
 - (d) With neat circuit diagram, explain how to convert a practical voltage source into an equivalent practical current source.
 - (e) Explain the concept of “duality” in electric circuit with one example.
4. Attempt any THREE of the following : 12
- (a) A series R-L-C circuit has $R = 5\ \Omega$, $L = 10\ \text{mH}$ and $C = 15\ \mu\text{F}$. Calculate :
 - (i) Resonant frequency
 - (ii) Q-factor of the circuit
 - (iii) Bandwidth (iv) Voltage magnification. Explain the “Current Magnification” in parallel resonant circuit consisting of inductive branch (RL) in parallel with a
 - (b) pure capacitor (C). Derive equation for it.

- (c) Draw waveform of three-phase voltages. Draw phasor diagram for these voltages. Write equations for instantaneous values of these voltages. Express these voltages in polar form.
- (d) State and explain "Reciprocity theorem".

5. Attempt any TWO of the following :

12

- (a) A coil having resistance of 5Ω and an inductance of 0.2 H is connected in parallel with a series combination of 10Ω resistor and $80 \mu\text{F}$ capacitor. If supply voltage is 230 V , 50 Hz , determine :
- Total circuit impedance.
 - Total current taken by the circuit.
 - Power factor of the circuit.
 - Branch currents.
 - Power consumed by the circuit.
- (b) Using mesh analysis, find current in 5Ω resistor in the network shown in Fig. 5(b).

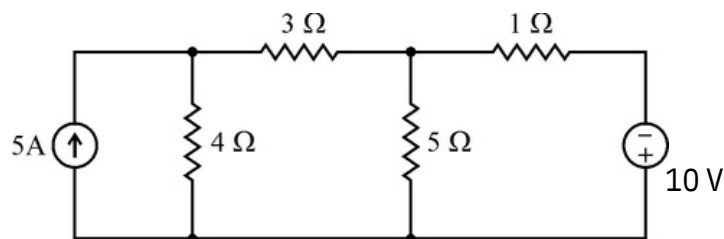


Fig. No. 5 (b)

- (c) Find the current in 5Ω resistor in the network shown in Fig. 5(c) by using Thevenin's theorem.

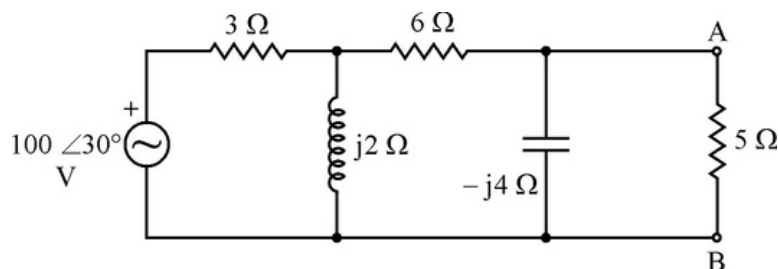


Fig. No. 5 (c)

6. Attempt any TWO of the following :

12

- (a) For a series R-L-C circuit consisting of $R = 5 \Omega$, $L = 0.01 \text{ H}$ and $C = 10 \mu\text{F}$ supplied with 230 V, 50 Hz supply, determine :
- Circuit impedance
 - Circuit current
 - Circuit power factor
 - Active power
 - Reactive power
 - Apparent power
- (b) A star connected capacitive load is supplied from 3 ϕ , 415 V, 50 Hz supply. If the line current is 15 A and total 3 ϕ power taken from supply is 30 kW , find :
- Power factor
 - Resistance in each phase
 - Capacitance in each phase.
- (c) Determine the voltage 'V' across 5Ω resistor in network shown in Fig. 6(c) using superposition theorem.

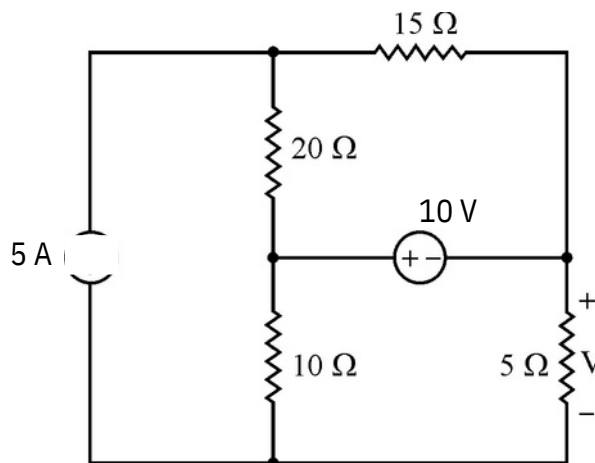


Fig. No. 6 (c)

Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

1 Attempt any TEN of the following: 20

1 a) Define Conductance and Susceptance related to AC circuit and state their units.

Ans:-

Conductance (G):

It is defined as the real part of the admittance (Y).

½ Mark for

It is also defined as the ability of the purely resistive circuit to pass the alternating current.

definition

½ Mark for
unit

OR

It is also defined as the ratio of resistance to the square of the impedance.

In general, Conductance, $G = \frac{1}{Z^2}$ siemen. Its unit is **siemen (S)**.

Susceptance (B):

It is imaginary part of the admittance (Y).

½ Mark for

It is defined as the ability of the purely reactive circuit (purely capacitive or purely inductive) to admit alternating current.

definition

½ Mark for
unit

OR


It is also defined as the ratio of reactance to the square of the impedance.

In general, Susceptance (B) = $\frac{1}{Z^2}$ siemen. Its unit is **siemen (S)**.

1 b) Draw power triangle for R-L series circuit. Write equation of power in rectangular form.

Ans:

1 Mark for
power
triangle

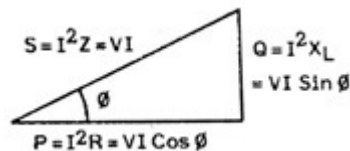

1 Mark for
equation

$$S = P + jQ$$

$$VI = VI \cos \phi + j VI \sin \phi$$

$$I^2 Z = IR^2 + j I^2 X_L$$

1 c) Express an instantaneous value of an alternating current varying sinusoidally in terms of its maximum value, frequency and time.

Ans:

where, $i =$ Instantaneous value = $I_m \sin(\omega t \pm \Phi)$ amp

1 Mark for
equation

$I_m =$ Maximum value

$\omega =$ Angular frequency in rad/sec = $2\pi f$

$f =$ frequency in cycles/sec or Hz

$t =$ time in sec

$\Phi =$ phase angle

1 Mark for
terms

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

- 1 d) State relationship between line and phase values of voltage and current in balanced delta connection.

Ans:

Balanced Delta Connection:

1 Mark

i.e

1 Mark

$$i.e \quad \frac{V_L}{\sqrt{3}} = \frac{V_P}{1}$$

- 1 e) Distinguish clearly between loop and mesh.

Ans:

Distinction between Loop & Mesh:

Sr. No.	Loop	Mesh
1	A loop is any closed path in a circuit, in which no node is encountered more than once	A mesh is a loop that has no other loops inside of it
2	Every loop is not a mesh	Every mesh is a loop
3	Loops are used in a more general way for circuit analysis	Meshes are used to analyze planar circuits

1 Mark for each of any two points = 2 Marks

- 1 f) State the value of internal resistance of (i) Ideal Voltage Source and (ii) Ideal Current Source.

Ans:

Value of Internal Resistance of Ideal Voltage Source $R_s = 0$

Value of Internal Resistance of Ideal Current Source $R_s = \infty$

1 Mark each

- 1 g) State Norton's Theorem.

Ans:

Norton's Theorem:

Any two terminal circuit having number of linear impedances and sources (voltage, current, dependent, independent) can be represented by a simple equivalent circuit consisting of a single current source I_N in parallel with an impedance Z_N across the terminals, where the source current I_N is equal to the short circuit current caused by internal sources when the two terminals are short circuited and the value of the parallel impedance Z_N is equal to the impedance of the circuit while looking back into the circuit across the two terminals, when the internal independent voltage sources are replaced by short-circuits and independent current sources by open circuits.

2 Marks for correct statement

- 2 Attempt any THREE of the following:**


12

- 2 a) With neat diagram, explain the phasor representation of sinusoidal quantity.

Ans:

Phasor Representation of Sinusoidal Quantity:

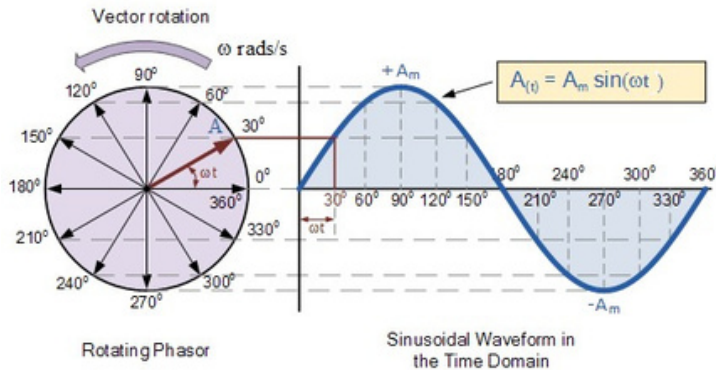**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**



2 Marks for diagram

OR Equivalent Figure

When number of waveforms are drawn in the same figure, the complexity of diagram increases and it becomes very difficult to extract the information from the waveforms. Therefore, to extract the same information, simplified alternate approach is preferred, called “Phasor representation of Sinusoidal quantity”.

2 Marks for explanation

A sinusoidal quantity is represented by a rotating vector or rotating phasor “A” whose length is equal to the amplitude of the quantity “Am”, as shown above. The points on the waveform are represented by the positions of the phasor during rotation drawn from the same reference point. The phasor making an angle of “ ωt ” with respect to positive x-axis reference, represents the instantaneous value of the quantity at an angle of “ ωt ” from its zero value, as shown above. In fact, the vertical component of the phasor represents the magnitude of the quantity at that particular instant. From the above diagram, it is clear that the vertical component of the phasor is “ $A_m \sin(\omega t)$ ” which is the instantaneous value of the quantity at instant “ ωt ”.


The speed of rotation of the phasor is equal to ω rad/sec where $\omega = 2\pi f$.

One rotation of the phasor corresponds to one cycle of the alternating waveform as shown in figure.

- 2 b) For a parallel circuit consisting of an inductive branch (RL) in parallel with a capacitive branch (RC), draw phasor diagram and derive equation for resonant frequency.

Ans:

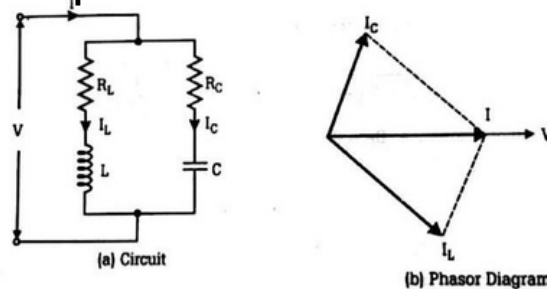Parallel Resonance in RL-RC parallel circuit:



1 Mark for phasor diagram

Parallel Resonance for RL-RC Parallel Circuit

The circuit diagram and phasor diagram is as shown in the figure. Under parallel resonance (anti-resonance) condition, the circuit will take an input current (I) in phase with the applied voltage (V). At resonance, the circuit impedance becomes purely resistive in spite of presence of L & C and the circuit power factor becomes unity.

Model Answers

Winter – 2019 Examinations

Subject & Code: Electrical Circuits (22324)

The admittance of inductive branch is:

$$-\frac{1}{j\omega L}$$

The admittance of capacitive branch is:

$$\frac{1}{-j\omega C}$$

Total admittance of the parallel circuit:

$$\left[\frac{1}{-\frac{1}{j\omega L}} + \frac{1}{\frac{1}{-j\omega C}} \right]$$

$$\left[-\frac{1}{\omega L} + \frac{1}{\omega C} \right]$$

3 Marks for
stepwise
derivation

At resonance, $\omega = \omega_r$ (anti-resonant angular frequency), the reactive term must be zero.

$$\left[-\frac{1}{\omega_r L} + \frac{1}{\omega_r C} \right]$$

$$\frac{-1}{\omega_r L} + \frac{1}{\omega_r C}$$

$$\frac{-1}{\omega_r L} + \frac{1}{\omega_r C}$$

$$\left[\frac{-1}{\omega_r L} + \frac{1}{\omega_r C} \right]$$

$$\left[\frac{-1}{\omega_r L} + \frac{1}{\omega_r C} \right]$$

$$-\frac{1}{\omega_r L}$$

$$\sqrt{-\frac{1}{\omega_r L}} \text{ rad/sec}$$

$$\omega_r \text{ Anti-resonant frequency} = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{LC}}$$

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

- 2 c) With the help of neat phasor diagram, derive the relationship between line and phase values of voltage in balanced star connection.

Ans:

Relationship Between Line voltage and Phase Voltage in Balanced Star Connection:

Let V_R, V_Y and V_B be the phase voltages.

V_{RY}, V_{YB} and V_{BR} be the line voltages.

The line voltages are expressed as:

$$V_{RY} = V_R - V_Y$$

$$V_{YB} = V_Y - V_B$$

$$V_{BR} = V_B - V_R$$

In phasor diagram, the phase voltages are drawn first with equal amplitude and displaced from each other by 120° . Then line voltages are drawn as per the above equations. It is seen that the line voltage V_{RY} is the phasor sum of phase voltages V_R and $-V_Y$. We know that in parallelogram, the diagonals bisect each other with an angle of 90° .

Therefore in $\triangle OPS$, $\angle P = 90^\circ$ and $\angle O = 30^\circ$.

$$[OP] = [OS] \cos 30^\circ$$


$$\text{Since } [OP] = V_L/2 \text{ and } [OS] = V_{ph}$$

$$\frac{V_L}{2} = V_{ph} \cos 30^\circ$$

Thus **Line voltage = $\sqrt{3}$ (Phase Voltage)**

- 2 d) State the equivalent delta connection for star connection of three resistances R_1, R_2 & R_3 with proper equations.

Ans:

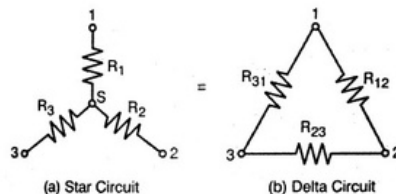

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

1 Mark for phasor diagram

3 Marks for stepwise derivation

1 mark for circuit diagram +

1 mark for each of 3 equations = 4 Marks

- 3 Attempt any THREE of the following:


12

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

3 a) For series R-L-C circuit, draw neat circuit diagram. State the conditions for RLC series ckt. Draw phasor diagram and voltage triangle impedance triangle for any 1 condition.

Ans:

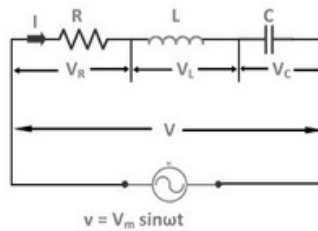Circuit Diagram for R-L-C Series Circuit:



½ Mark for circuit diagram + ½ Mark for each of 3 conditions = 2 Mark

Conditions for R-L-C Series Circuit:

(i) When $X_L > X_C$: Phase angle is positive and circuit will be inductive. In other words, in such a case, the circuit current I will lag behind the applied voltage V by angle ϕ .




(ii) When $X_L < X_C$: Phase angle is negative and circuit will be capacitive. In other words, in such a case, the circuit current I leads the applied voltage V by angle ϕ .

(iii) When $X_L = X_C$: The circuit is purely resistive. In other word circuit current I and applied voltage V will be in phase i.e. The circuit will have unity power factor.

1 Mark for phasor diagram +




Phasor Diagram, Voltage Triangle & Impedance Triangle:

(i) Condition $X_L > X_C$

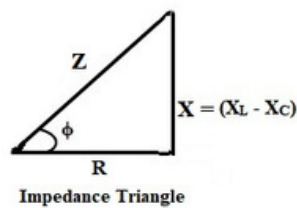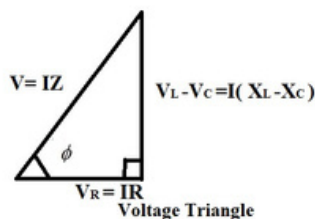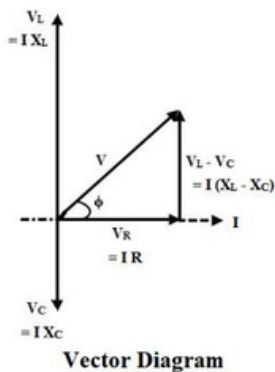

½ Mark each for voltage triangle & impedance triangle for any one condition = 2 Mark

(ii) Condition $X_L < X_C$

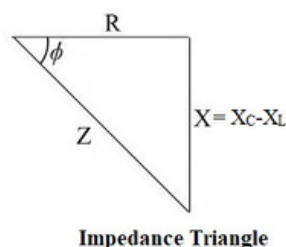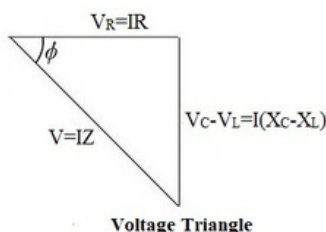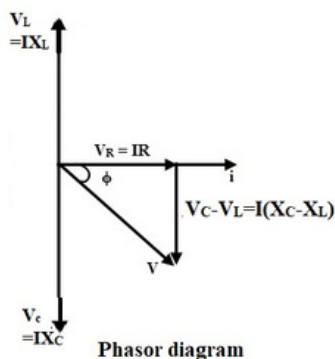

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

3 b) State any four properties of Parallel Resonance.

Ans:

Properties of Parallel Resonance:

1. At resonance, the parallel RLC circuit behaves as purely resistive circuit.
2. At resonance, the Parallel RLC circuit power factor is unity.
3. At resonance, the parallel RLC circuit offers maximum total impedance

$$Z = L/CR$$

4. At resonance, parallel RLC circuit draws minimum current from source,

$$\frac{1}{Z}$$

5. At resonance, in parallel RLC circuit, current magnification takes place.

6. The Q-factor for parallel resonant circuit is,

$$-v-$$


7. Parallel RLC resonant circuit is Rejecter circuit.

1 Mark for each of any four properties = 4 Marks

3 c) With neat labeled diagram, explain unbalanced star connected load.

Ans:

Unbalanced Star connected Load:

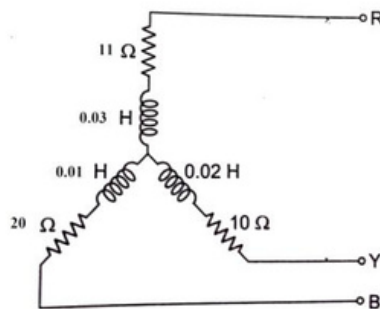

1. When the magnitudes and phase angles of three impedances are differ from each other, then it is called as unbalanced load.
2. Phase angles of impedance are not equal.
3. For unbalanced load, the phase voltage v is of the line voltage.
4. All the voltages are fixed and line currents will not be equal nor will have a phase difference.

1 Mark for labeled circuit diagram + 3 Marks for explanation (any 3 points) = 4 Marks


3 d) With neat circuit diagram, explain how to convert a practical voltage source into an equivalent practical current source.

Ans:

Conversion of practical voltage source into equivalent practical current source:


Let V_S be the practical voltage source magnitude and Z_V be the internal series impedance of the voltage source.
 I_S be the equivalent practical current source magnitude and Z_I be the internal parallel impedance of current source.

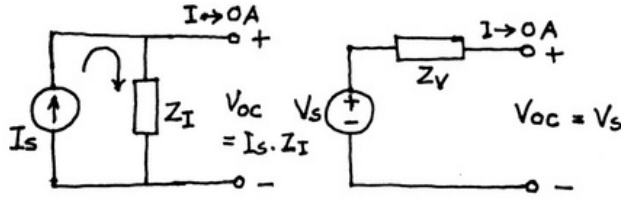**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**



1 Mark for each equation = 4 Marks

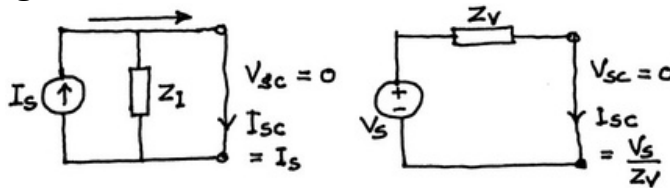The open circuit terminal voltage of voltage source is $V_{OC} = V_S$
 The open circuit terminal voltage of current source is $V_{OC} = I_S \square Z_I$
 Therefore, we get $V_S = I_S \square Z_I$ (1)



The short circuit output current of voltage source is $I_{SC} = V_S / Z_V$
 The short circuit output current of current source is $I_{SC} = I_S$
 Therefore, we get $I_S = V_S / Z_V$ (2)
 Therefore, we get $V_S = I_S \square Z_V$ (3)
 On comparing eq. (1) and (3), it is clear that $Z_I = Z_V = Z$ (4)

Thus the internal impedance of both the sources is same, and the magnitudes of the source voltage and current are related by Ohm's law, $V_S = I_S \square Z$

3 e) Explain the concept of “duality” in electric circuit with one example.

Ans:

Concept of duality:

When the two circuit elements are represented by mathematical equations of similar nature, then these elements are called dual elements of each other.

Examples:

- (i) A resistance is represented by mathematical equation based on Ohm's law as, $R = V/I$ and the conductance is represented by $G = I/V$. 1 Mark
- (ii) A voltage across an inductance is represented by $v = L \frac{di}{dt}$ and the current through a capacitor is represented by $i = C \frac{dv}{dt}$. 1 Mark

On comparing the above equations we can form pairs of dual elements or quantities: 1 Mark

Resistance $R \leftrightarrow$ Conductance G
 Inductance $L \leftrightarrow$ Capacitance C
 Voltage $v \leftrightarrow$ Current i

OR

OR

Similarly, we can apply this concept to electric circuits and say that when the two circuits are represented by similar mathematical equations, then such circuits are called dual circuits of each other.


Consider a series R-L-C circuit, the voltage equation can be written as:

$v(t) = R.i(t) + L \frac{di(t)}{dt} + \int i(t) dt$ (1) 1 Mark

Consider a parallel R-L-C circuit, the current equation can be written as:

$i(t) = \frac{v(t)}{R} + C \frac{dv(t)}{dt} + \int v(t) dt$ (2) 1 Mark

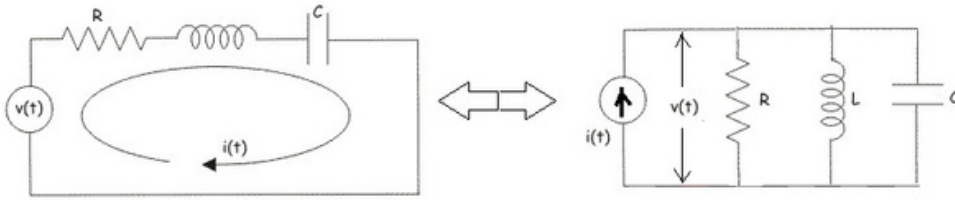**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**



1 Mark

On comparing equations (1) & (2), it is seen that both the equations are integro-differential equations of similar kind. Therefore, the two circuits are dual circuits. The dual element pairs are:

- Voltage source $v(t) \leftrightarrow$ Current source $i(t)$
- Resistance $(R) \leftrightarrow$ Conductance $(G = 1/R)$
- Inductance $(L) \leftrightarrow$ Capacitance (C)
- Series Circuit \leftrightarrow Parallel circuit

1 Mark

Examples of duality in electric circuit

- voltage – current
- parallel circuit – series circuit
- resistance – conductance
- voltage division – current division
- impedance – admittance
- capacitance – inductance
- reactance – susceptance
- short circuit – open circuit
- Kirchhoff's Voltage law – Kirchhoff's Current law
- Mesh – Node
- Thevenin's theorem – Norton's theorem

4 Attempt any THREE of the following.

12

4 a) A series R-L-C circuit has $R = 5\Omega$, $L = 10\text{mH}$ and $C = 15\mu\text{F}$. Calculate:

- (i) Resonant frequency
- (ii) Q-factor of the circuit
- (iii) Bandwidth
- (iv) Voltage Magnification.

Ans:

Data Given:

$R = 5\Omega$, $L = 10\text{mH} = 10^{-2}$, $C = 15\mu\text{F} = 15 \times 10^{-6}$,

i) Resonant frequency:

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{10^{-2} \times 15 \times 10^{-6}}}$$

$$= 410.94 \text{ Hz}$$

1 Mark for
each bit
= 4 Marks

ii) Quality factor of circuit:

$$Q \text{ factor} = \frac{\omega L}{R} = \frac{2\pi f_r L}{R}$$

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

= _____
= **5.16**

iii) **Bandwidth:**
Bandwidth = _____

= _____ = **79.64 Hz**


iv) **Voltage Magnification:**

Q factor = $\sqrt{\frac{L}{C}}$ _____
= _____
= **5.16**

4 b) Explain the “Current Magnification” in parallel resonant circuit consisting of inductive branch (RL) in parallel with a pure capacitor (C). Derive equation for it.

Ans:

Current Magnification in Parallel Resonant (RL||C) Circuit:

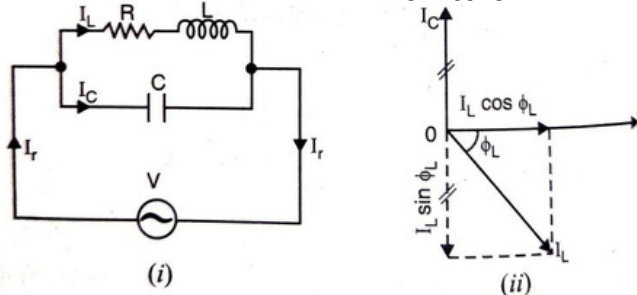

1 Mark for diagram

Current Magnification:

The Current Magnification or quality factor or Q-factor of parallel resonant circuit is defined as the ratio of the current circulating between two branches of the circuit to the current taken by the parallel circuit from the source. 1 Mark

Current Magnification = Q-factor = _____

At parallel resonance, the circulating current is I_C and circuit condition is,

$$I_C - I_L = 0$$

_____ (1)

Total circuit input current, $I = I_r$

If the circuit impedance at resonance is Z , then

Substituting Z^2 from eq. (1),

2 Marks for stepwise derivation

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

$$\frac{V}{\sqrt{3}} \dots\dots\dots (2)$$

Now, circulating current $I_C = V/XC = \frac{V}{\sqrt{3}X_C}$

and input line current taken by circuit $I_r = \frac{V}{\sqrt{3}X_C}$

Current Magnification = Q-factor = $\frac{V}{I_C} = \sqrt{3}X_C$

Current Magnification = Q-factor = $\frac{V}{I_C} = \sqrt{3}X_C$

The Q-factor of a parallel resonant circuit can also be expressed in term of L and C.

Neglecting resistance R, the resonance frequency is given by;


$$f_r = \frac{1}{\sqrt{LC}}$$

Now,

$$\text{Current Magnification} = Q\text{-factor} = \frac{V}{I_C} = \frac{V}{\frac{V}{\sqrt{3}X_C}} = \sqrt{3}X_C$$

- 4 c) Draw waveform of three-phase voltages. Draw phasor diagram for these voltages. Write equations for instantaneous values of these voltages. Express these voltages in polar form.

Ans:

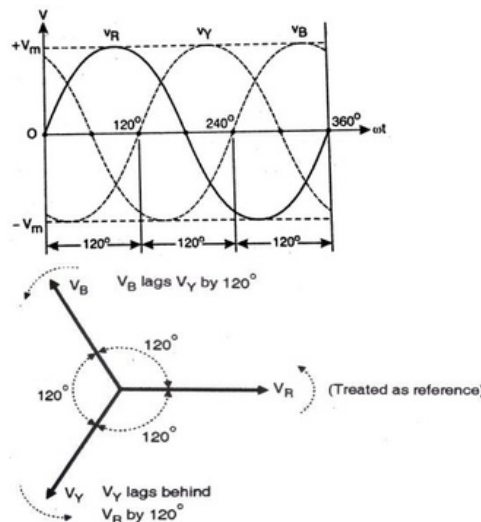

1 Mark for waveform

1 Mark for phasor diagram

The equations of three-phase voltages can be represented by,

$$v_R = V_m \sin \omega t$$

$$v_Y = V_m \sin(\omega t - 120^\circ)$$

$$v_B = V_m \sin(\omega t - 240^\circ) = V_m \sin(\omega t + 120^\circ)$$

1 Mark for equations

Polar Form:

Let V be the RMS value of the phase voltage, $V = \frac{V_m}{\sqrt{2}}$

-
-
-

□

1 Mark for polar form


**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

4 d) State and explain “Reciprocity theorem”.

Ans: Reciprocity theorem : Reciprocity Theorem states that in any bilateral network if a voltage source V in one branch, say branch „A“, produces a current I in another branch, say branch „B“, then if the voltage source V is moved from the branch A to the branch B, it will cause the same current I in the first branch „A“, where the voltage source has been replaced by a short circuit.

2 Marks for

statement

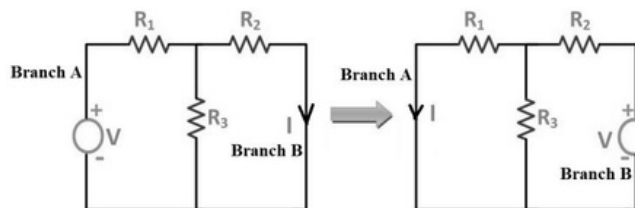

Steps for Solving a Network Utilizing Reciprocity Theorem:

Step 1: Firstly, select the branches, say A and B, between which reciprocity has to be established.

Step 2: The current I_1 in the branch B is obtained using any conventional network analysis method, when the source is in the branch A.

2 Marks for
explanation

Step 3: The voltage source is moved to branch B.

Step 4: The current I_2 in the branch A, where the voltage source was existing earlier, is calculated.

Step 5: It is seen that the current I_1 obtained in the previous connection, i.e., in step 2

and the current I_2 which is calculated when the source is moved to branch B

The first step is applicable to each other. It is applicable only to single source networks and not in the multi-source network. The network where reciprocity theorem is applied should be linear and consist of resistors, inductors, capacitors and coupled circuits. The circuit should not have any time-varying elements.

5 **Attempt any TWO of the following:**

12

5 a) A coil having resistance of 5Ω and an inductance of 0.2 H is connected in parallel with a series combination of 10Ω resistor and $80 \mu\text{F}$ capacitor. If supply voltage is 230 V , 50 Hz , determine:

- 1) Total circuit impedance
- 2) Total current taken by the circuit
- 3) Power factor of the circuit
- 4) Branch currents
- 5) Power consumed by the circuit

Ans:

Data Given: Branch I: $R_1 = 5 \Omega$ and $L = 0.2 \text{ H}$

Branch II: $R_2 = 10 \Omega$ and $C = 80 \mu\text{F} = 80 \times 10^{-6} \text{ F}$

$V = 230 \text{ V}$, $f = 50 \text{ Hz}$

(i) Total circuit impedance (Z):

Inductive reactance $X_L = 2\pi fL$

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

$= 2 \times \pi \times 50 \times 0.2$ ½ Mark for XL
XL = 62.83 Ω
 Capacitive reactance $X_C = 1 / (2\pi fC)$ ½ Mark for XC
 $X_C = 1 / (2\pi \times 50 \times 80 \times 10^{-6})$
XC = 39.79 Ω
 Branch 1 Impedance $Z_1 = (5 + j62.83) \Omega = 63.03 \angle 85.45^\circ \Omega$
 Branch 2 Impedance $Z_2 = (10 - j39.79) \Omega = 41.03 \angle -75.89^\circ \Omega$
 Since impedances are in parallel, total circuit impedance is given by,

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

Total circuit impedance Z 1 Mark for Z

(ii) Total current (I) :
 Total Current (I): $I = \frac{V}{Z}$ 1 Mark for I

Angle between V and I is $\{0 - 47.37\} = -47.37^\circ$ 1 Mark for pf

(iii) Power factor of the circuit (cos φ) :
 $\cos \phi = \cos(-47.37^\circ) = 0.68$ leading

(iv) Branch Currents: ½ Mark for each branch current = 1 Mark

$$I_1 = \frac{V}{Z_1} = \frac{230}{63.03} = 3.65 \text{ A}$$

$$I_2 = \frac{V}{Z_2} = \frac{230}{41.03} = 5.61 \text{ A}$$

(v) Power consumed by the circuit: 1 Mark for P
 $P = V \times I \times \cos \phi = 230 \times 2.44 \times 0.68$
P = 381.62 watt

5 b) Using mesh analysis, find current in 5 Ω resistor in the network shown in Fig. 5(b).


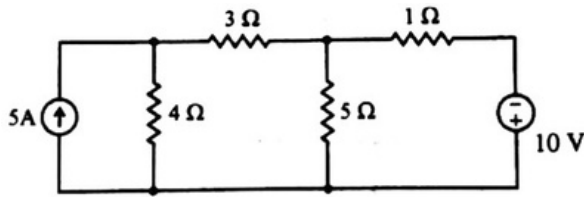


Fig. No. 5 (b)

Ans:

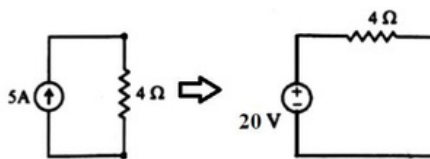A) Converting current source of 5A, 4Ω into equivalent voltage source:
 Emf of voltage source $V = I \times R = 5 \times 4 = 20$ volt
 Internal resistance of voltage source = internal resistance of current source = 4 Ω




1 Mark

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

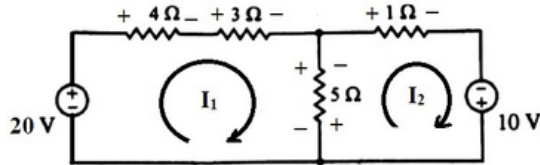B) Modified circuit:

Replacing current source with equivalent voltage source, the modified circuit diagram is as shown below. The mesh currents can be marked as shown.



C) Mesh Analysis:

By applying KVL to Mesh 1:

..... (1)

1 Mark for Eq. (1)

By applying KVL to Mesh 2:

.....(2)

1 Mark for Eq. (2)

Expressing eq.(1) and (2) in matrix form,

$$\begin{bmatrix} \quad & \quad \\ \quad & \quad \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \quad \\ \quad \end{bmatrix}$$

1 Mark for Eq. in matrix form

By Cramer's rule,

$$\frac{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}}{\begin{vmatrix} \quad & \quad \\ \quad & \quad \end{vmatrix}} = \frac{\quad}{\quad}$$

½ Mark for I1

½ Mark for I2

Current flowing through resistance of 5 Ω = I₂ – I₁ = 4.68 – 3.62 = 1.06 A in the direction of I₂

1 Mark

- 5 c) Find the current in 5 Ω resistor in the network shown in Fig. 5(c) by using Thevenin's theorem.


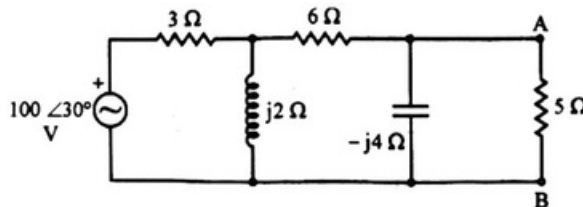


Fig. No. 5 (c)

Ans:

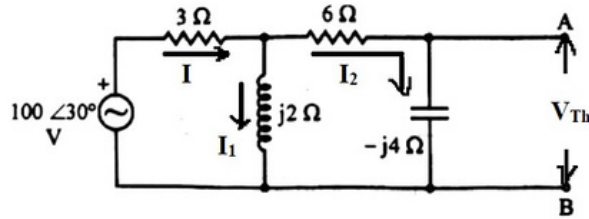1) Determination of Thevenin's equivalent voltage V_{Th}:

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**



2 Marks for
stepwise
calculation
of V_{Th}

Thevenin's voltage V_{Th} is the open circuit voltage between load terminals A & B. It is seen that it is the voltage across capacitor.

The net impedance across 100V source is given by,
 $Z = 3 + (j2) \parallel (6-j4)$

$$\begin{aligned} \text{The total current } I &= \frac{V}{Z} = \frac{100 \angle 30^\circ}{3 + (j2) \parallel (6-j4)} \\ \text{The capacitor current } I_2 &= \frac{I \cdot (6-j4)}{6} \\ &= \frac{7.5 \angle 107^\circ \cdot (6-j4)}{6} \\ &= 7.5 \angle 107^\circ = (-2.2 + j7.17) \text{ A} \end{aligned}$$


Thevenin's voltage $V_{Th} = (-j4)I_2 = (4 \angle 90^\circ)(7.5 \angle 107^\circ)$

$V_{Th} = 30 \angle 197^\circ \text{ volt} = (-28.69 - j8.77) \text{ volt}$

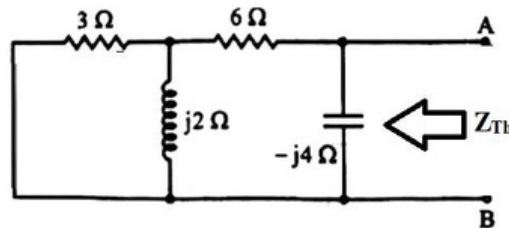2) Determination of Thevenin's Equivalent Impedance Z_{Th} :


It is the impedance seen between the open circuited terminals A & B with all internal independent voltage sources replaced by short circuit and all internal independent current sources by open circuit.

2 Marks for
stepwise
calculation
of Z_{Th}



$$\begin{aligned} Z_{Th} &= (-j4) \parallel \{6 + (3 \parallel j2)\} \\ &= (-j4) \parallel \left\{6 + \left(\frac{3 \cdot j2}{3 + j2}\right)\right\} = (-j4) \parallel \left\{6 + \left(\frac{6j}{5 + j2}\right)\right\} \\ &= (-j4) \parallel \left\{6 + \left(\frac{56.3 \angle 90^\circ}{56.3 \angle 21.8^\circ}\right)\right\} = (-j4) \parallel \{6 + 0.92 + j1.38\} \\ &= (-j4) \parallel \{6.92 + j1.38\} = (-j4) \parallel \{7.056 \angle 11.28^\circ\} \\ &= \underline{\underline{(2.02 - j3.23) \Omega}} \end{aligned}$$

3) Thevenin's Equivalent Circuit:

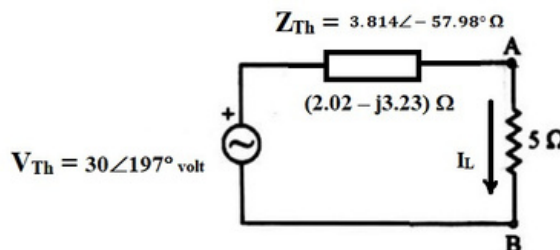

1 Mark for
Thevenin's
Eq. circuit

1 Mark for I_L

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

The current in 5Ω resistor is given by,

$$I_L = \frac{V}{Z} = \frac{230}{318.31} = 0.7226 \text{ A}$$

6 Attempt any TWO of the following: 12

6 a) For a series R-L-C circuit consisting of $R = 5\Omega$, $L = 0.01 \text{ H}$ and $C = 10 \mu\text{F}$ supplied with 230 V, 50 Hz supply, determine:

- i) Circuit impedance
- ii) Circuit current
- iii) Circuit power factor
- iv) Active power
- v) Reactive power
- vi) Apparent power

Ans:

Data Given: $R = 5 \Omega$, $L = 0.01 \text{ H}$, $C = 10 \mu\text{F} = 10 \times 10^{-6} \text{ F}$
 $V = 230 \text{ V}$, $f = 50 \text{ Hz}$

1 Mark for
each bit
= 6 Marks

(i) Circuit Impedance:

$$= 3.142 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 318.31 \Omega$$

$$Z = R + j(X_L - X_C) = 5 + j(3.142 - 318.31)$$

$$\mathbf{Z = (5 - j 315.168) \Omega = 315.21 \angle -89.1^\circ \Omega}$$

(ii) Circuit current:

$$\text{Circuit current } I = \frac{V}{Z} = \frac{230}{315.21} = \mathbf{0.73 \angle 89.1^\circ \text{ A}}$$

Circuit power factor:

(iii) Circuit Power factor angle $\phi = 89.1^\circ$ leading

$$\text{Circuit power factor } \cos \phi = \cos(89.1^\circ) = \mathbf{0.016 \text{ (leading)}}$$

Active Power (P):

(iv) $P = VI \cos \phi = 230 \times 0.73 \times 0.016$

$$= \mathbf{2.6864 \text{ W}}$$

(v) Reactive Power (Q):

$$Q = VI \sin \phi = 230 \times 0.73 \times \sin(89.1^\circ)$$

$$= \mathbf{167.88 \text{ VAR}}$$

(vi) Apparent Power (S):

$$\text{Apparent Power} = S = VI = 230 \times 0.73 = 167.9 \text{ VA}$$

6 b) A star connected capacitive load is supplied from 3ϕ , 415V, 50Hz supply. If the line current is 15 A and total 3ϕ power taken from supply is 30 kW, find:

- i) Power factor
- ii) Resistance in each phase.
- iii) Capacitance in each phase

Ans:

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

Data Given: $V_L = 415V$, $f = 50Hz$, $I_L = 15A$, $P = 30\text{ kW} = 30000\text{ W}$

In Star connection,

$V_L = \sqrt{3} \times V_{Ph}$ and $I_L = I_{Ph}$

Therefore, $V_{Ph} = V_L / \sqrt{3} = 415 / \sqrt{3} = \mathbf{239.6\text{ Volt}}$.

And $I_L = I_{Ph} = \mathbf{15Amp}$.

Impedance per phase, $Z_{Ph} = V_{Ph} / I_{Ph} = 239.6 / 15$

$Z_{Ph} = \mathbf{15.97\ \Omega}$

1 Mark for
ZPh

i) Power factor:

Total three-phase power is given by,

$P = 3V_{Ph} I_{Ph} \cos\phi$ Or $P = \sqrt{3}V_L I_L \cos\phi$

$30 \times 10^3 = 3 \times 239.6 \times 15 \times \cos\phi$

Therefore,

$\cos\phi = 30 \times 10^3 / (3 \times 239.6 \times 15)$

$\phi \cos\phi = \mathbf{2.78\text{ !!!!!!!!!}}$

Since maximum value of $\cos\phi = 1$, here is data mismatch !!!!!!!!!

Assuming total 3 ϕ power as 3 kW instead of 30 kW,

$\cos\phi = 3 \times 10^3 / (3 \times 239.6 \times 15)$

$\cos\phi = \mathbf{0.278\text{ leading}}$

$\phi^{-1} = \cos(0.278) = \mathbf{73.84}$

1 Mark for
 $\cos\phi$
1 Mark for ϕ

(NOTE: Examiner is requested to award appropriate marks to the student for any other suitable assumption of data and if attempted to solve)

ii) Resistance in each phase:

Resistance per phase (R_{ph}) = $Z_{ph} \times \cos\phi = 15.97 \times 0.278$

$R_{ph} = \mathbf{4.44\ \Omega}$

1 Mark for
RPh

iii) Reactance in each phase:

Reactance per phase (X_{ph}) = $Z_{ph} \times \sin\phi = 15.97 \times \sin(73.84^\circ)$

$X_{ph} = \mathbf{15.34\ \Omega}$

1 Mark for
XPh

Since capacitive reactance $X_C = X_{ph} =$

Capacitance in each phase $C =$ _____

1 Mark for C

F

6 c) Determine the voltage „V“ across 5 Ω resistor in the network shown in Fig. 6(c) using superposition theorem.

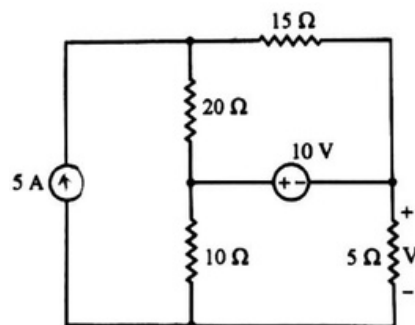



Fig. No. 6 (c)

Ans:

**Model Answers
Winter – 2019 Examinations
Subject & Code: Electrical Circuits (22324)**

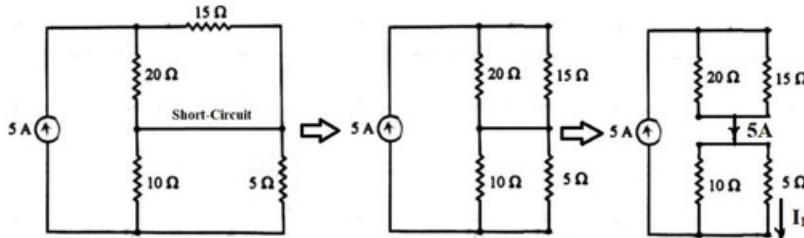(A) Consider current source of 5A acting alone:

The 10V source is replaced by short-circuit (S.C.)




1 Mark for diagram
1 Mark for I1

The total source current of 5A is divided and then flows through 5Ω & 10Ω
The current flowing through 5Ω is given by current division formula as,

$$I_1 = 5 \times \left\{ \frac{10}{10+5} \right\} = \mathbf{3.33A \text{ (Downward)}}$$

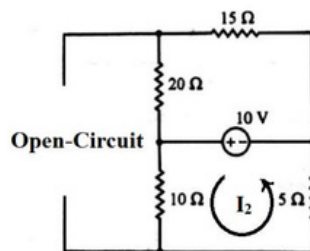(B) Consider voltage source of 10V acting alone:

The 5A source is replaced by open-circuit (O.C.)



1 Mark for diagram
1 Mark for I2

The current in lower mesh and flowing through 5Ω is given by,

$$I_2 = 10 / (10+5) = \mathbf{0.67A \text{ (Upward)}}$$

(C) Total current in 5Ω resistor:

By Superposition theorem, the current through 5Ω due to both sources, assuming downward current positive and upward current negative, is given by,

$$\mathbf{I = I_1 - I_2 = (3.33 - 0.67) = 2.66A \text{ (Downward)}}$$

1 Mark for I

Voltage across 5Ω resistor is given by,

$$V = 5(I) = 5(2.66) = 13.3 \text{ volt}$$

1 Mark for V

$$\mathbf{V = 13.3 \text{ volt}}$$